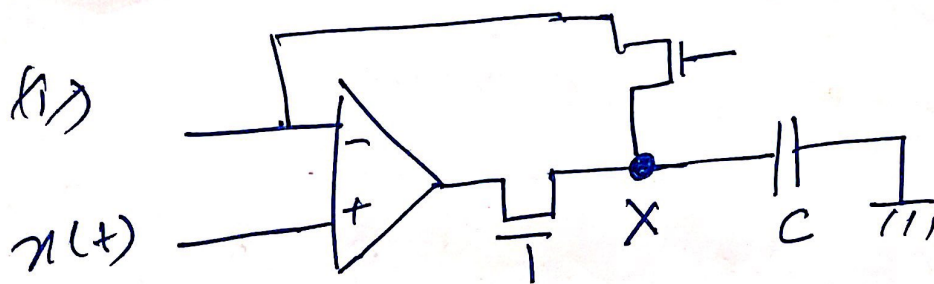


Tutorial 1

Q4] (A)





Whenever the MOSFETs are given high ~~not~~ gate voltage, they will become conducting, and hence the potential at $X = x(t)$ where $\tau =$ time when MOSFET is on.

Whenever the MOSFET is switched off, the capacitor will cause the voltage at X to be held a constant, til the next time that the MOSFET is switched on.


(i) When $T_p \ll T_s$, we can assume the value of $x(t)$ to be constant in that interval.

\therefore The voltage at X will be constant for a duration of T_s and equal to the value $x(nT_s)$. i.e. sample & hold. on convolving with Fig 4

b/p of ideal sampler :-

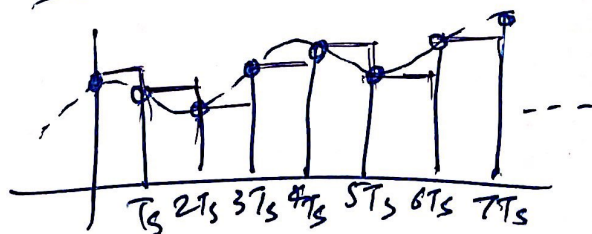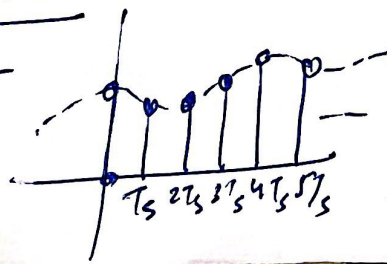

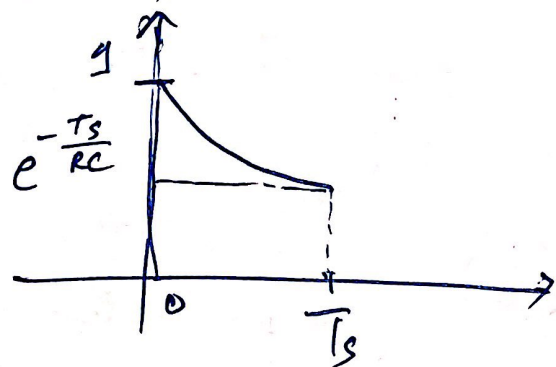(ii) The degradation will be that the capacitor will not hold the value constant. The value will decay with time constant RC . Basically the sampling will be ideal, but we will convolve with



(iii) The voltage at x will follow $x(t)$ til T_p and then hold on for $(T_s - T_p)$.

