

**EE334**  
**Mutually coupled circuits and  
transformers**


**Prof. A. M. Kulkarni**

**Electrical Engineering Dept.  
IITB, Mumbai**




**28<sup>th</sup> January, 2020.**

## 1. Dot convention in coupled circuits

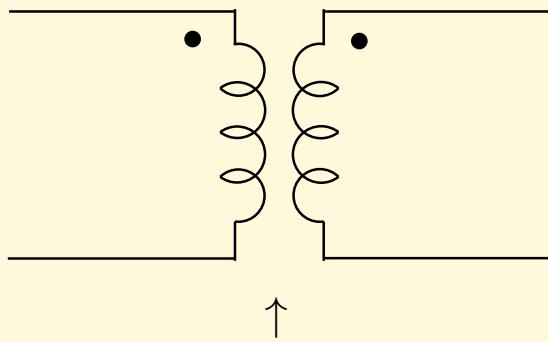

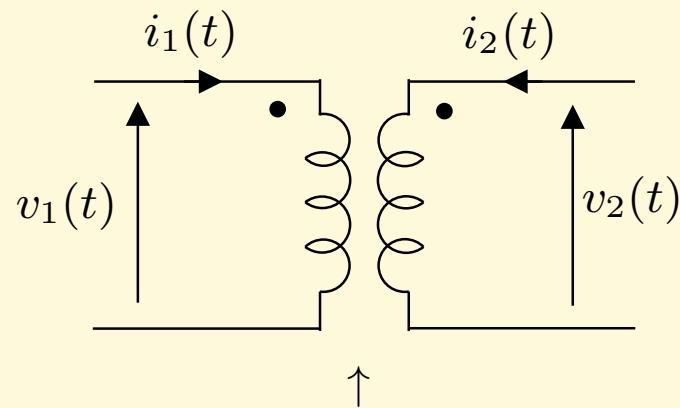
$$\begin{bmatrix} L_{11} & M \\ M & L_{22} \end{bmatrix}$$




$$\begin{bmatrix} v_1(t) \\ v_2(t) \end{bmatrix} = \frac{d}{dt} \begin{bmatrix} L_{11} & M \\ M & L_{22} \end{bmatrix} \begin{bmatrix} i_1(t) \\ i_2(t) \end{bmatrix}$$

$$\begin{bmatrix} v_1(t) \\ v_2(t) \end{bmatrix} = \frac{d}{dt} \begin{bmatrix} \psi_1(t) \\ \psi_2(t) \end{bmatrix}$$

## Dot convention in coupled circuits

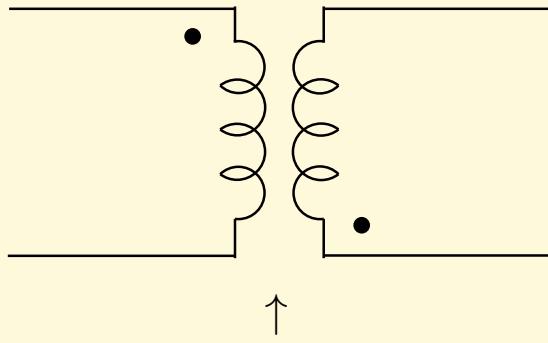

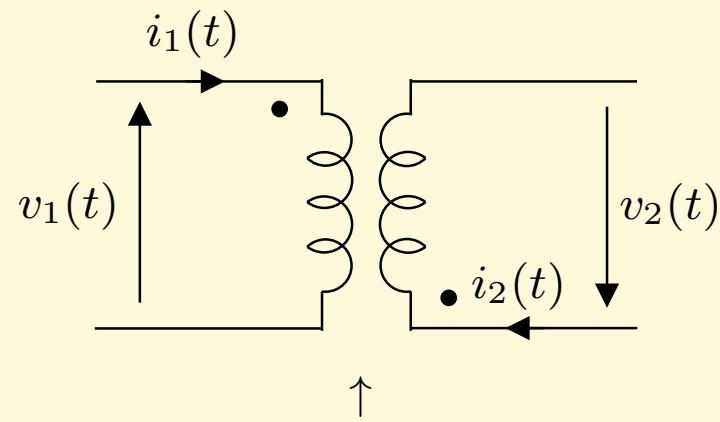
$$\begin{bmatrix} L_{11} & M \\ M & L_{22} \end{bmatrix}$$



$$\begin{bmatrix} v_1(t) \\ v_2(t) \end{bmatrix} = \frac{d}{dt} \begin{bmatrix} L_{11} & M \\ M & L_{22} \end{bmatrix} \begin{bmatrix} i_1(t) \\ i_2(t) \end{bmatrix}$$

$$\begin{bmatrix} v_1(t) \\ v_2(t) \end{bmatrix} = \frac{d}{dt} \begin{bmatrix} \psi_1(t) \\ \psi_2(t) \end{bmatrix}$$

## 2. Ideal transformer

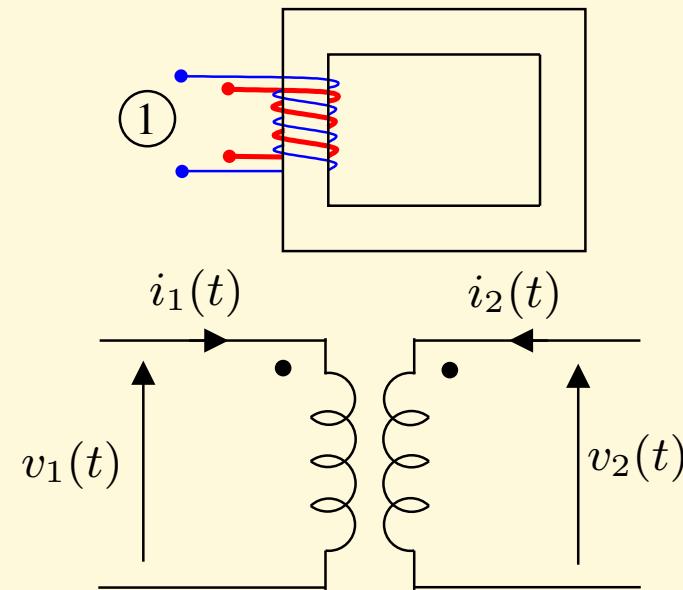

## Ideal transformer

Using Faraday's law:

$$\begin{bmatrix} v_1(t) \\ v_2(t) \end{bmatrix} = \frac{d}{dt} \begin{bmatrix} \psi_1(t) \\ \psi_2(t) \end{bmatrix} = \frac{d}{dt} \begin{bmatrix} L_{11} & M \\ M & L_{22} \end{bmatrix} \begin{bmatrix} i_1(t) \\ i_2(t) \end{bmatrix}$$

where,  $\psi_1$  and  $\psi_2$  are the flux links in the coils 1 and 2, given as:

## Ideal transformer

**Using Faraday's law:**

$$\begin{bmatrix} v_1(t) \\ v_2(t) \end{bmatrix} = \frac{d}{dt} \begin{bmatrix} \psi_1(t) \\ \psi_2(t) \end{bmatrix} = \frac{d}{dt} \begin{bmatrix} L_{11} & M \\ M & L_{22} \end{bmatrix} \begin{bmatrix} i_1(t) \\ i_2(t) \end{bmatrix}$$

where,  $\psi_1$  and  $\psi_2$  are the flux links in the coils 1 and 2, given as:

$$\frac{\psi_1}{N_1} = \phi_1 = \frac{L_{11}}{N_1} i_1 + \frac{M}{N_1} i_2 \quad (1)$$

$$\frac{\psi_2}{N_2} = \phi_2 = \frac{M}{N_2} i_1 + \frac{L_{22}}{N_2} i_2 \quad (2)$$

## Ideal transformer

**Using Faraday's law:**

$$\begin{bmatrix} v_1(t) \\ v_2(t) \end{bmatrix} = \frac{d}{dt} \begin{bmatrix} \psi_1(t) \\ \psi_2(t) \end{bmatrix} = \frac{d}{dt} \begin{bmatrix} L_{11} & M \\ M & L_{22} \end{bmatrix} \begin{bmatrix} i_1(t) \\ i_2(t) \end{bmatrix}$$

where,  $\psi_1$  and  $\psi_2$  are the flux links in the coils 1 and 2, given as:

$$\frac{\psi_1}{N_1} = \phi_1 = \frac{L_{11}}{N_1} i_1 + \frac{M}{N_1} i_2$$

$$\frac{\psi_2}{N_2} = \phi_2 = \frac{M}{N_2} i_1 + \frac{L_{22}}{N_2} i_2$$

For all  $i_1(t)$  and  $i_2(t)$  in **Ideal transformers**  $\phi_1 = \phi_2$

$$\frac{v_1}{v_2} = \frac{N_1}{N_2} \text{ also } L_{11} = \frac{N_1}{N_2} M \quad L_{22} = \frac{N_2}{N_1} M \quad L_{11} L_{22} = M^2$$

### 3. Ideal transformer in phasor domain

In sinusoidal steady-state, the ideal transformer's equations are:

$$\begin{bmatrix} \bar{V}_1 \\ \bar{V}_2 \end{bmatrix} = j\omega \begin{bmatrix} L_{11} & M \\ M & L_{22} \end{bmatrix} \begin{bmatrix} \bar{I}_1 \\ \bar{I}_2 \end{bmatrix}$$

Under **open-circuit secondary**:  $\bar{I}_{oc} = \frac{\bar{V}_1}{j\omega L_{11}}$

## Ideal transformer in phasor domain contd...

In sinusoidal steady-state, the ideal transformer's equations are:

$$\begin{bmatrix} \bar{V}_1 \\ \bar{V}_2 \end{bmatrix} = j\omega \begin{bmatrix} L_{11} & M \\ M & L_{22} \end{bmatrix} \begin{bmatrix} \bar{I}_1 \\ \bar{I}_2 \end{bmatrix}$$

Under **open-circuit secondary**:  $\bar{I}_{oc} = \frac{\bar{V}_1}{j\omega L_{11}}$

Under loaded condition:

$$\bar{V}_1 = j\omega L_{11} \bar{I}_{1load} + j\omega M \bar{I}_{2load}$$

$$\bar{V}_1 = j\omega L_{11} \bar{I}_{1load} + j\omega \frac{N_2}{N_1} L_{11} \bar{I}_{2load}$$

$$\bar{V}_1 = j\omega L_{11} \left( \bar{I}_{1load} + \frac{N_2}{N_1} \bar{I}_{2load} \right) \quad (3)$$

## Ideal transformer in phasor domain contd...

$$\bar{V}_1 = j\omega L_{11} \left( \bar{I}_{1load} + \frac{N_2}{N_1} \bar{I}_{2load} \right)$$

Under **open-circuit secondary**:  $\bar{I}_{oc} = \frac{\bar{V}_1}{j\omega L_{11}}$

$$\left( \bar{I}_{oc} - \frac{N_2}{N_1} \bar{I}_{2load} \right) = \bar{I}_{1load}$$

---

If  $\bar{I}_{oc}$  is **negligible** compared to load currents, then

$$\bar{I}_{1load} = \left( -\frac{N_2}{N_1} \bar{I}_{2load} \right)$$


## MMF balance

Consider the equation  $\left( \bar{I}_{oc} - \frac{N_2}{N_1} \bar{I}_{2load} \right) = \bar{I}_{1load}$

Multiplying throughout by  $N_1$  and rearranging,


$$N_1 (\bar{I}_{1load} - \bar{I}_{oc}) = -N_2 \bar{I}_{2load}$$

For three winding transformer:

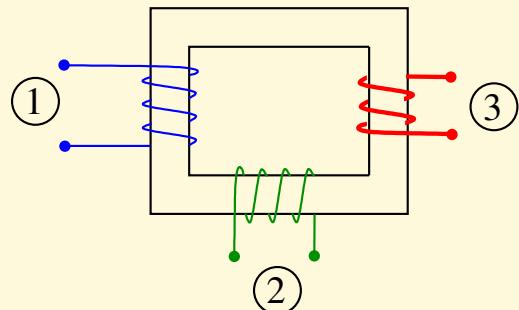

$$N_1 (\bar{I}_{1load} - \bar{I}_{oc}) = -N_2 \bar{I}_{2load} - N_3 \bar{I}_{3load}$$
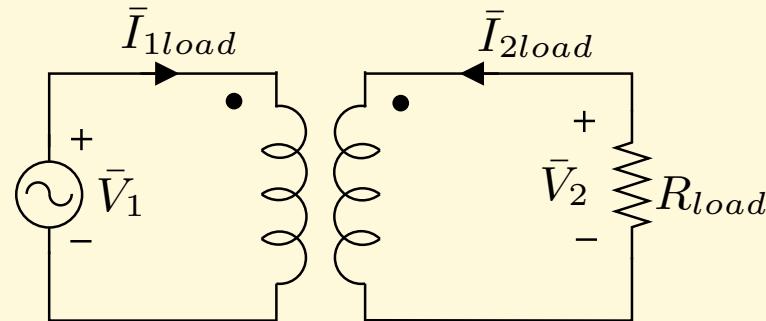
## Ideal transformer in phasor domain contd...



$$\begin{bmatrix} \bar{V}_1 \\ \bar{V}_2 \end{bmatrix} = j\omega \begin{bmatrix} L_{11} & M \\ M & L_{22} \end{bmatrix} \begin{bmatrix} \bar{I}_{1load} \\ \bar{I}_{2load} \end{bmatrix}$$


$$\bar{I}_{1load} = \left( \bar{I}_{oc} - \frac{N_2}{N_1} \bar{I}_{2load} \right)$$

Note:  $\bar{I}_{oc} = \frac{\bar{V}_1}{j\omega L_{11}}$  and  $\bar{I}_{2load} = \frac{-\bar{V}_2}{R_{load}}$


## Ideal transformer in phasor domain contd...

$$\bar{I}_{1load} = \left[ \frac{1}{j\omega L_{11}} + \frac{1}{R_{load} \left( \frac{N_1}{N_2} \right)^2} \right] \bar{V}_1$$

Original system:

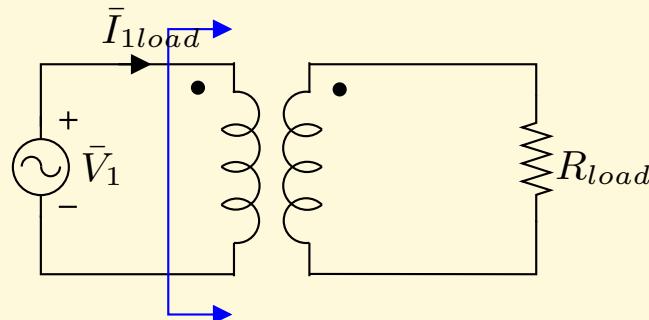


Equivalent system:

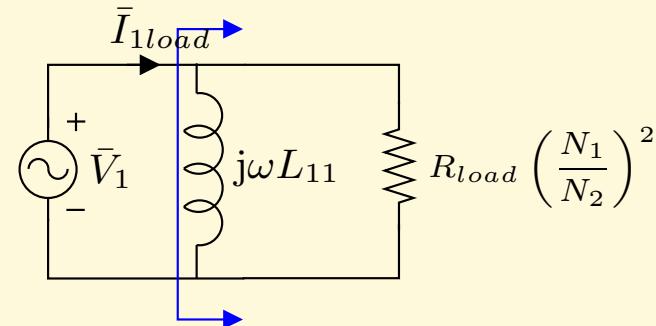

Note: above equivalent with ideal transformers **only**.
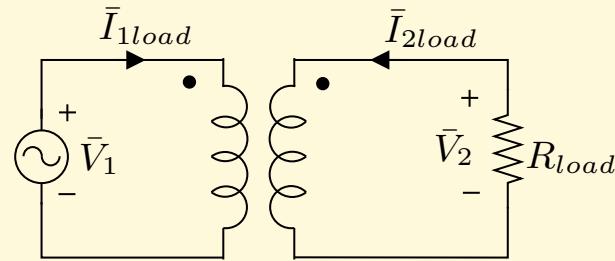
## Ideal transformer in phasor domain contd...



Note:  $\bar{I}_{1load} = \left( \bar{I}_{oc} - \frac{N_2}{N_1} \bar{I}_{2load} \right)$

For the above system:

$$\bar{V}_1 \bar{I}_1^* = \bar{V}_1 \left( \bar{I}_{oc} - \frac{N_2}{N_1} \bar{I}_{2load} \right)^*$$

$$\bar{V}_1 \bar{I}_1^* = \bar{V}_1 \bar{I}_{oc}^* - \frac{N_2}{N_1} \bar{V}_1 \bar{I}_{2load}^*$$

$$\bar{V}_1 \bar{I}_1^* = \bar{V}_1 \bar{I}_{oc}^* - \bar{V}_2 \bar{I}_{2load}^*$$

## Ideal transformer in phasor domain contd...

Also the real power is given by:


$$\bar{V}_1 \bar{I}_1^* = \bar{V}_1 \bar{I}_{oc}^* - \bar{V}_2 \bar{I}_{2load}^*$$

$$Re\{\bar{V}_1 \bar{I}_1^*\} = Re\{\bar{V}_1 \bar{I}_{oc}^* - \bar{V}_2 \bar{I}_{2load}^*\}$$

$$Re\{\bar{V}_1 \bar{I}_1^*\} = Re\{-\bar{V}_2 \bar{I}_{2load}^*\}$$

$$Re\{\bar{V}_1 \bar{I}_1^*\} = R_{load} |\bar{I}_{2load}|^2$$


## 4. Practical transformer

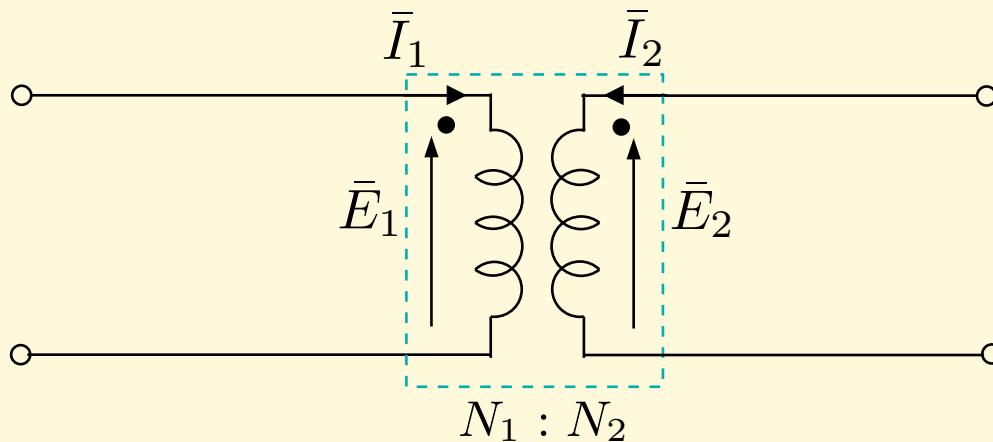

**Figure:** Ideal transformer ( $\bar{I}_{oc} = 0$ ).

$$\frac{\bar{E}_1}{\bar{E}_2} = \frac{N_1}{N_2}, \quad \frac{\bar{I}_1}{\bar{I}_2} = -\frac{N_2}{N_1}$$


## Practical transformer contd...

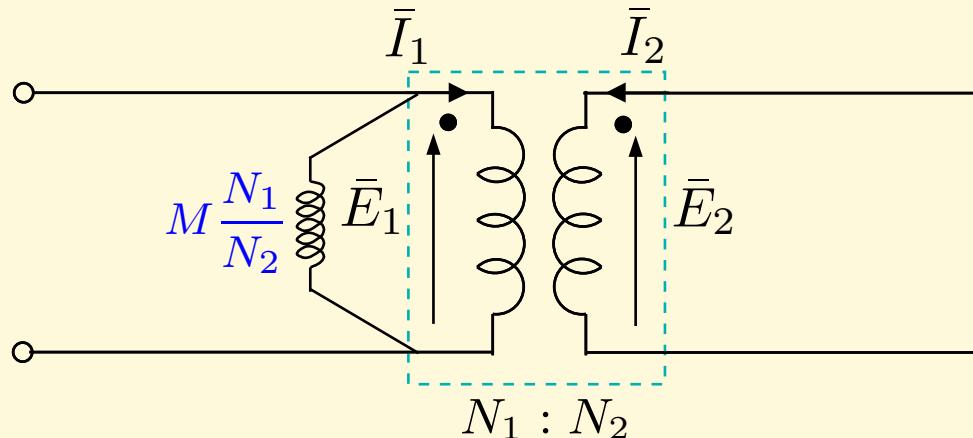

**Figure:** Ideal transformer ( $\bar{I}_{oc} \neq 0$ ).  
[Note:  $M \frac{N_1}{N_2}$  is in source side and draws  $\bar{I}_{oc}$  from the source.]

$$\frac{\bar{E}_1}{\bar{E}_2} = \frac{N_1}{N_2}, \quad \frac{\bar{I}_1}{\bar{I}_2} = -\frac{N_2}{N_1}$$


## Practical transformer contd...

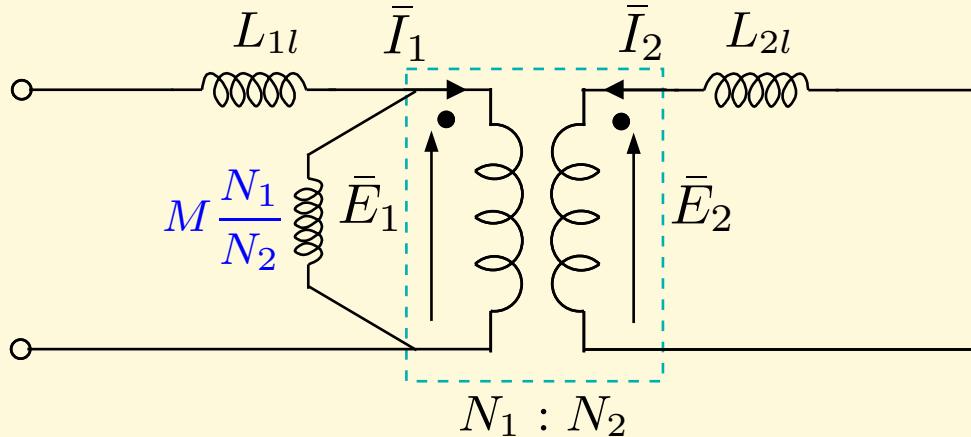

**Figure:** Practical transformer.  
[ $L_{1l}$  and  $L_{2l}$  are the leakage inductances of the windings.]

$$\frac{\bar{E}_1}{\bar{E}_2} = \frac{N_1}{N_2}, \quad \frac{\bar{I}_1}{\bar{I}_2} = -\frac{N_2}{N_1}$$


## Practical transformer contd...

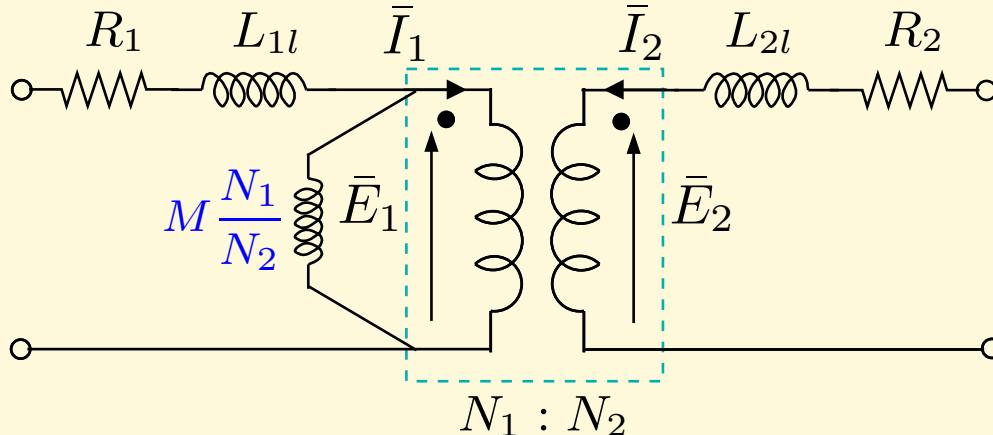

**Figure:** Practical transformer.  
[ $R_1$  and  $R_2$  abstracts the winding resistances.]

$$\frac{\bar{E}_1}{\bar{E}_2} = \frac{N_1}{N_2}, \quad \frac{\bar{I}_1}{\bar{I}_2} = -\frac{N_2}{N_1}$$

## Practical transformer contd...

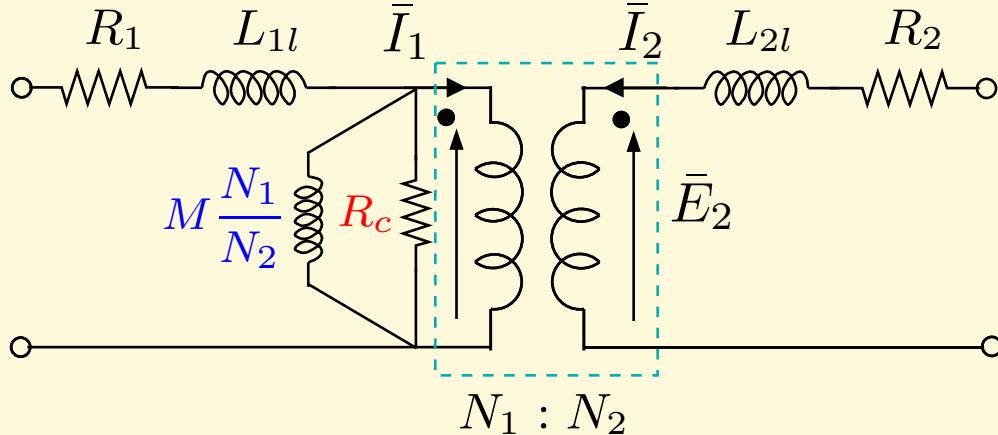

**Figure:** Practical transformer.  
[ $R_c$  abstracts core losses (eddy current and hysteresis losses).]

$$\frac{\bar{E}_1}{\bar{E}_2} = \frac{N_1}{N_2}, \quad \frac{\bar{I}_1}{\bar{I}_2} = -\frac{N_2}{N_1}$$


# Single phase 50 Hz transformer (low power ratings)



Name plate rating:  
2000 VA, 230 V/ 115 V, 50 Hz



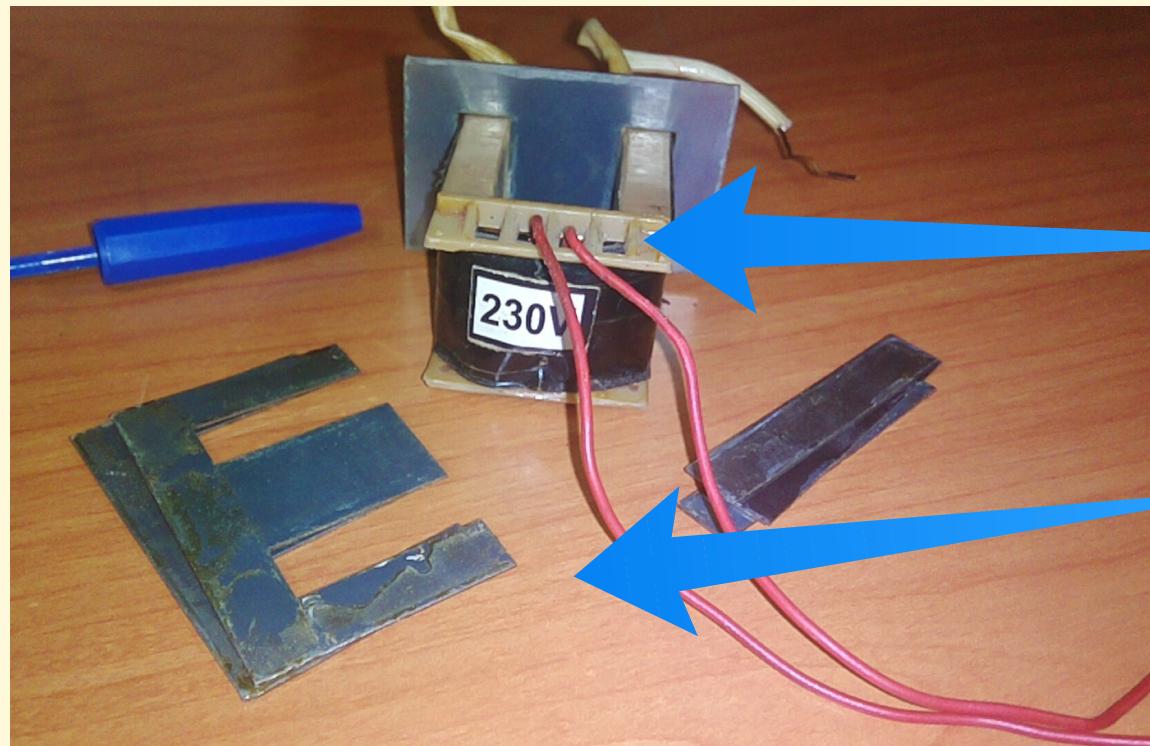
# Single phase 50 Hz transformer (low power ratings)



Bobbin holding  
both the windings

E-I laminated CRGO  
stacks (cold rolled  
grain-oriented steel)
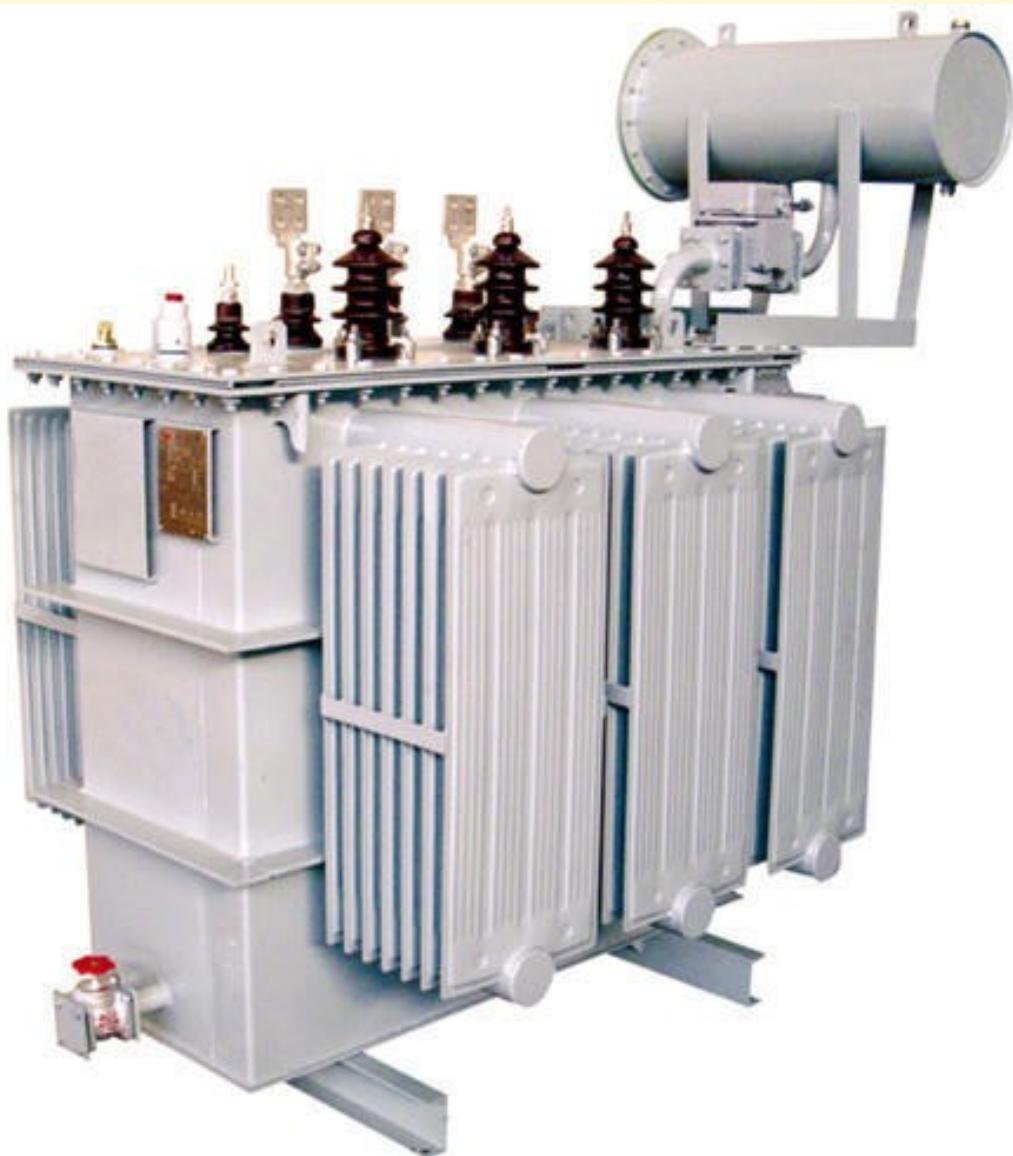
## Single phase 50 Hz transformer (high power ratings)




12.5 MVA, 33 kV/ 11 kV 50 Hz.


# Single phase 50 Hz transformer (high power ratings)


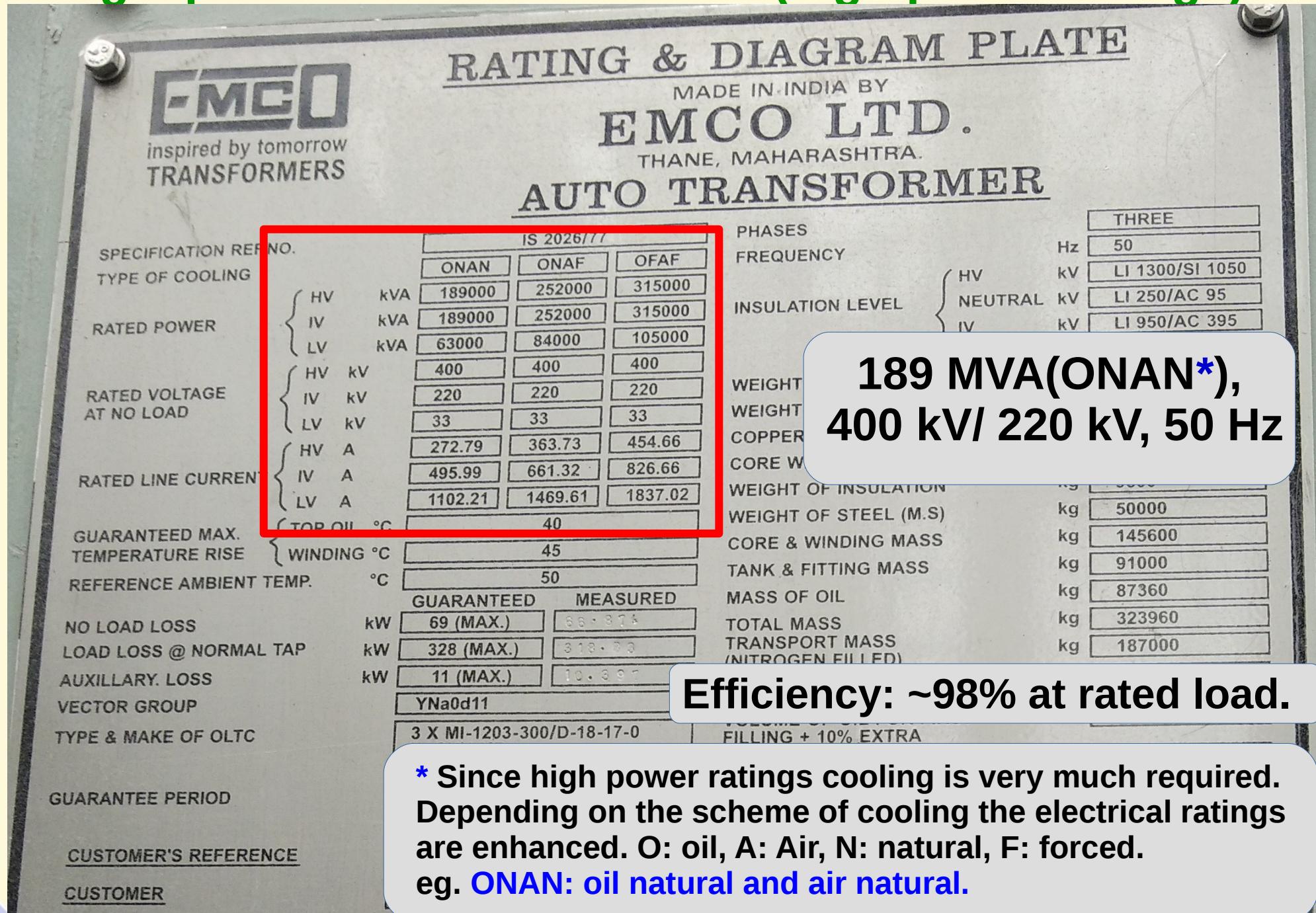
# Single phase 50 Hz transformer (high power ratings)




# Single phase 15 kHz transformer

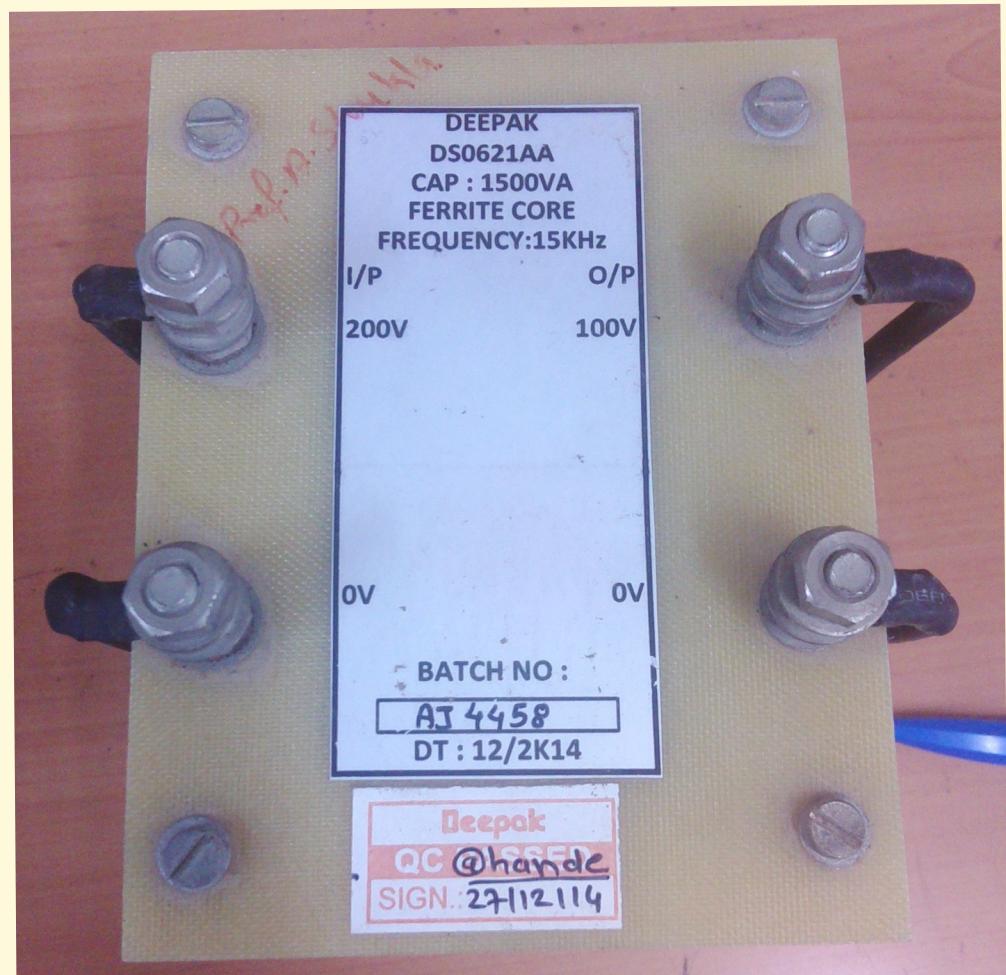


**1.5 kVA, 200 V/ 100 V, 15 kHz**

# Single phase 15 kHz transformer

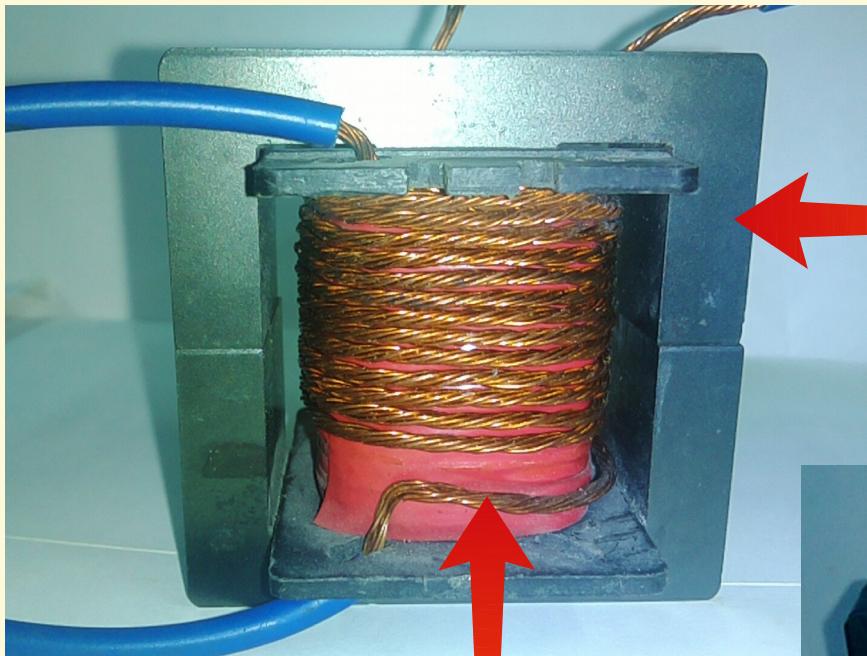


Litz wire, (stranded wire) for utilizing conductor cross section at high frequency


E-E Ferrite core

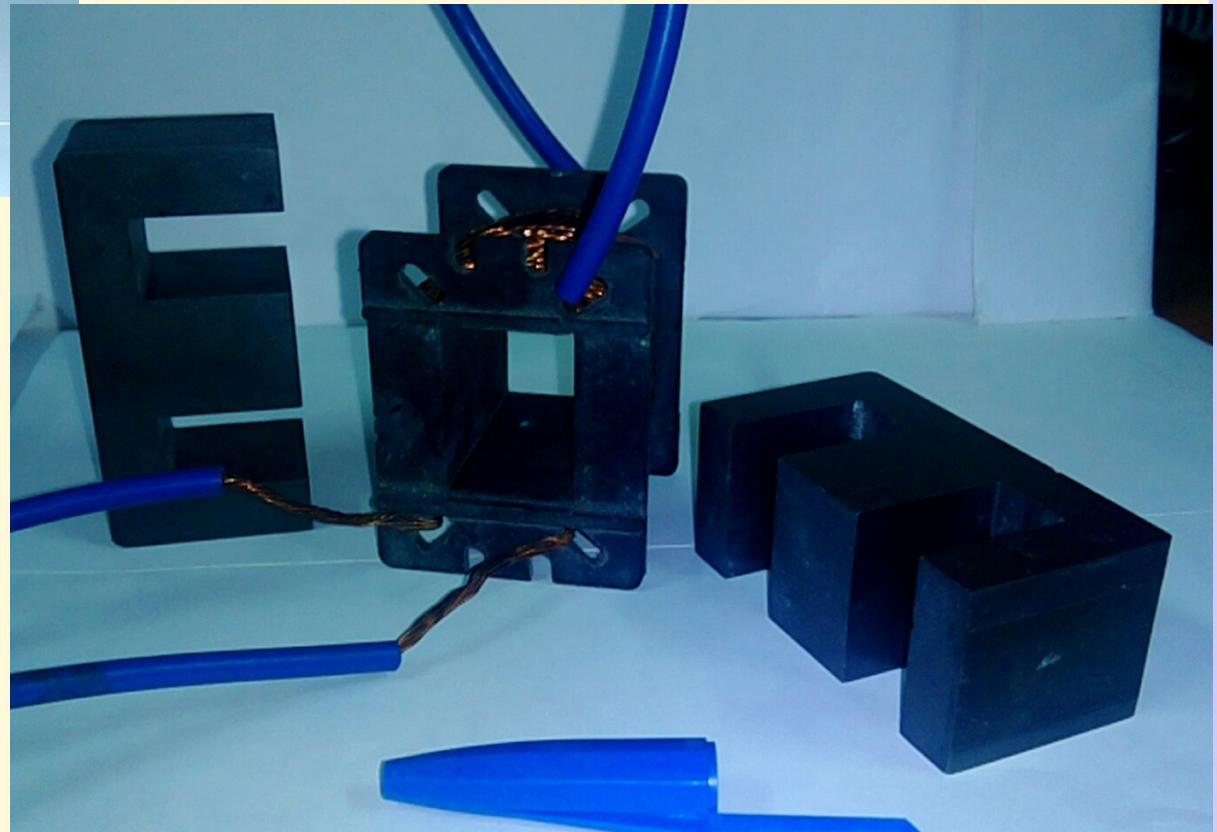
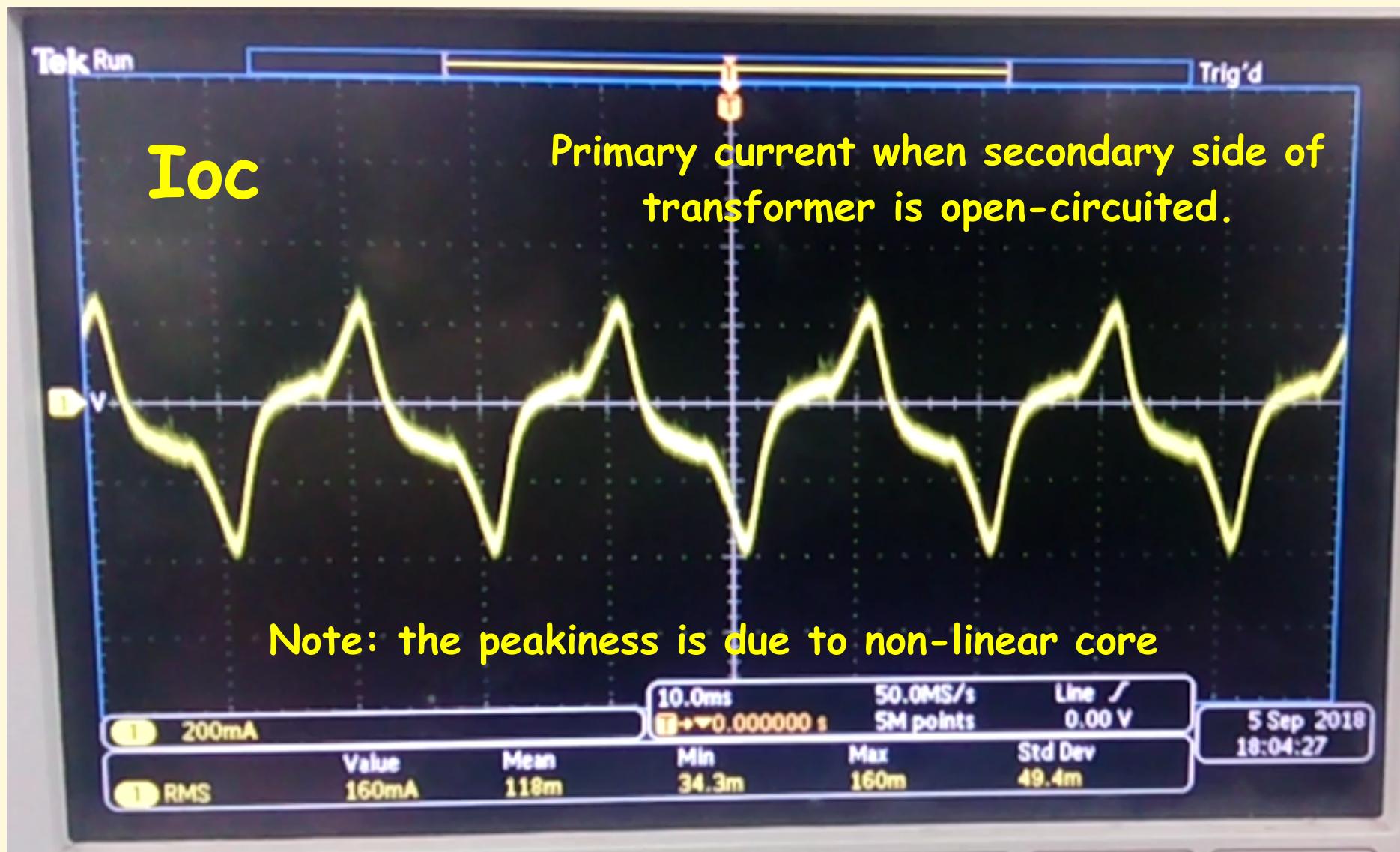
# Input current when secondary open-circuited.



## Auto transformer or variac

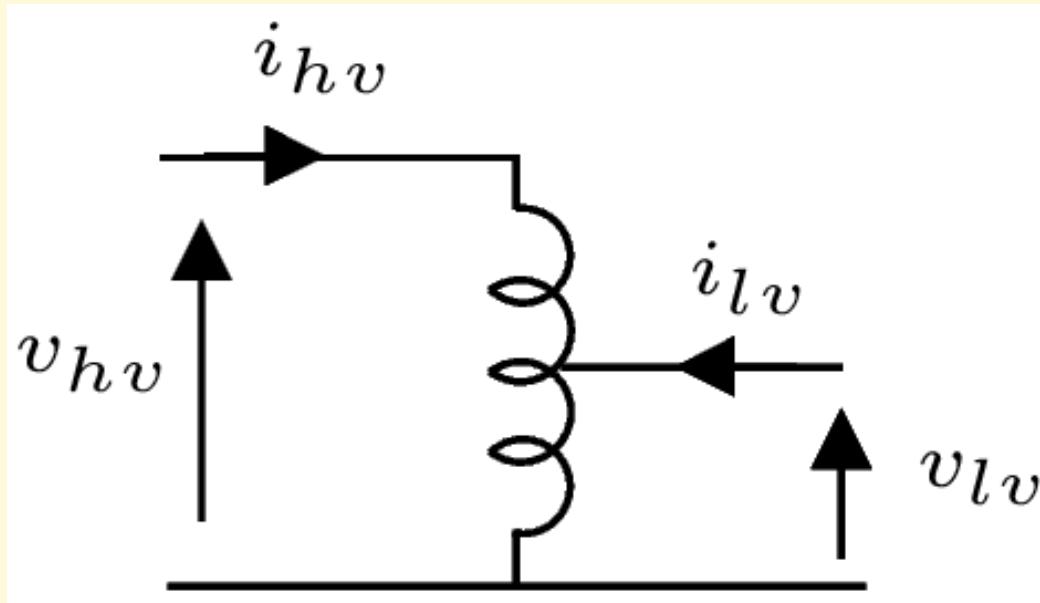


# **Isolation using transformer**

# Experiment for illustrating isolation


Case-1

Consider the following circuit

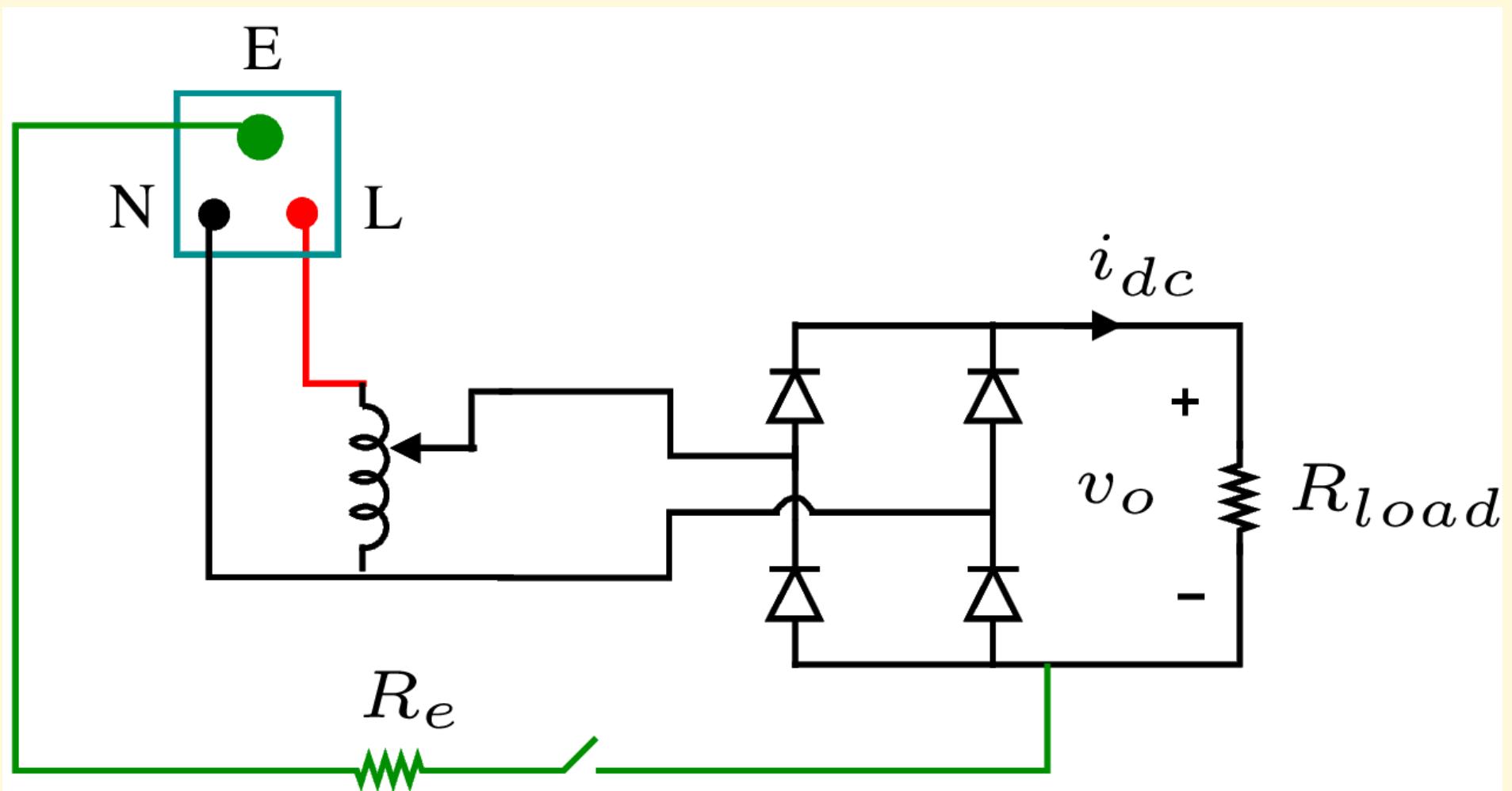

# Experiment for illustrating isolation


Case-1

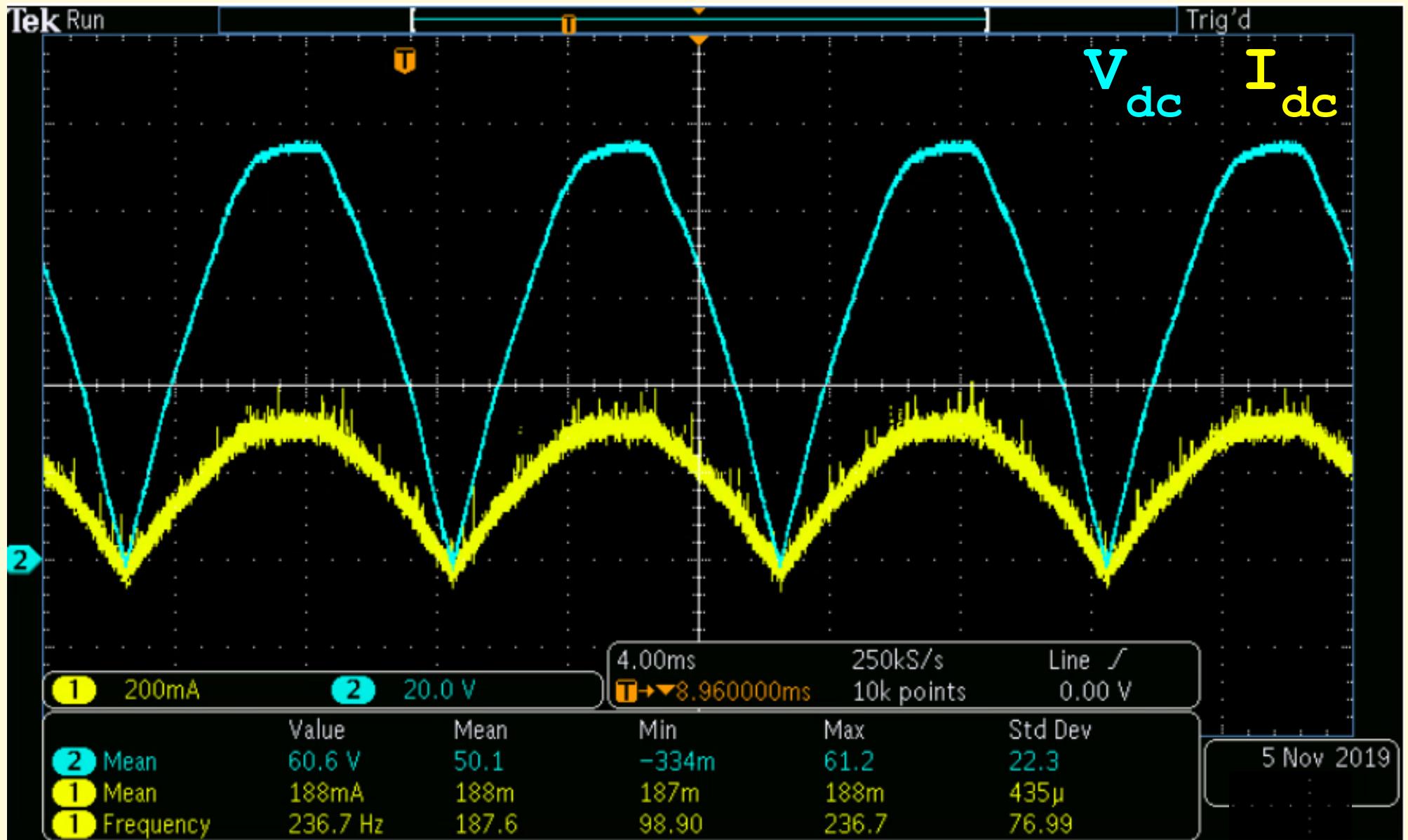

Negative bus not earthed

# Experiment for illustrating isolation

Case-1

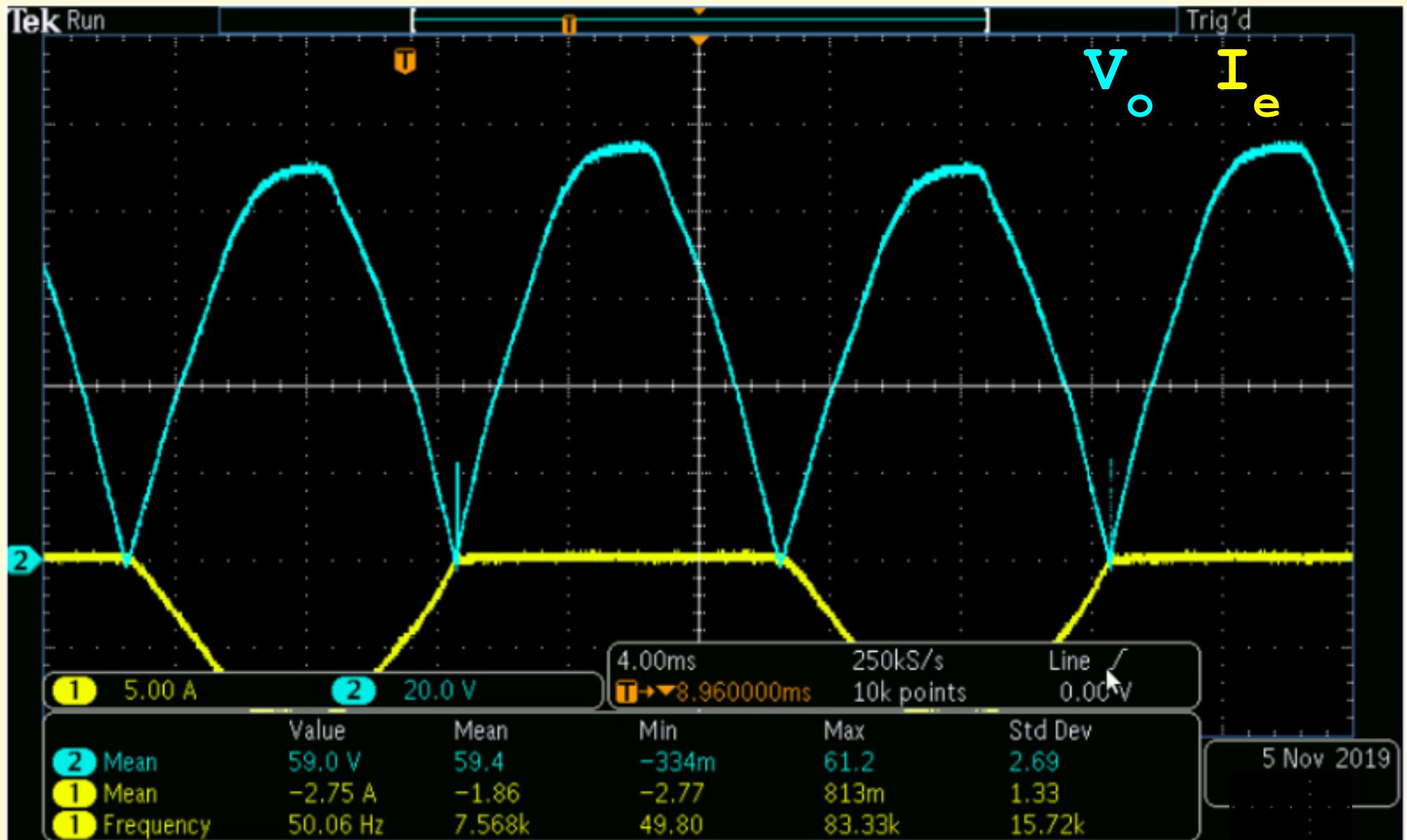


Negative bus earthed through a resistor
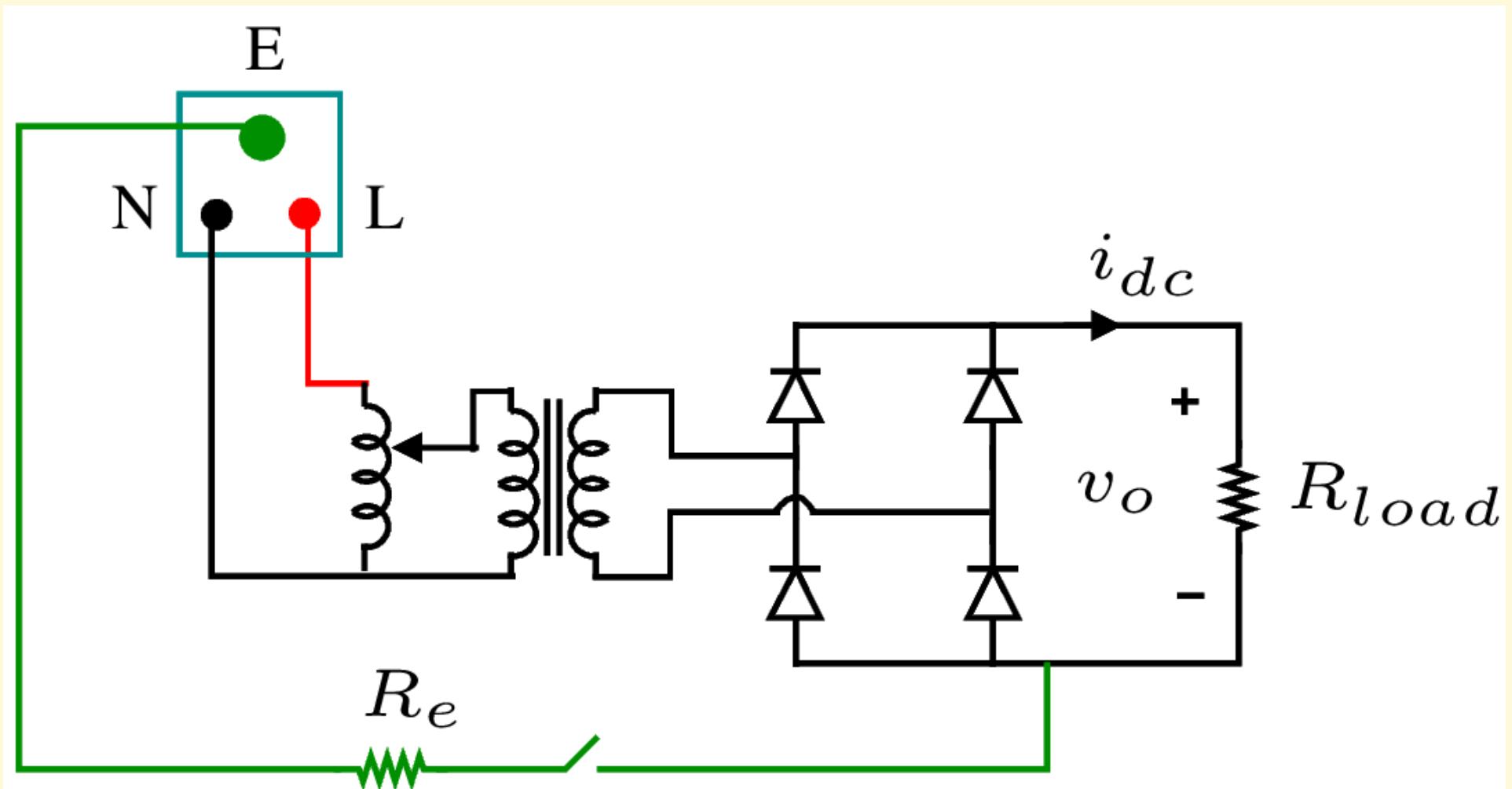
# Experiment for illustrating isolation


Case-2

Consider the previous circuit but with a isolation transformer:



# Experiment for illustrating isolation


Case-2

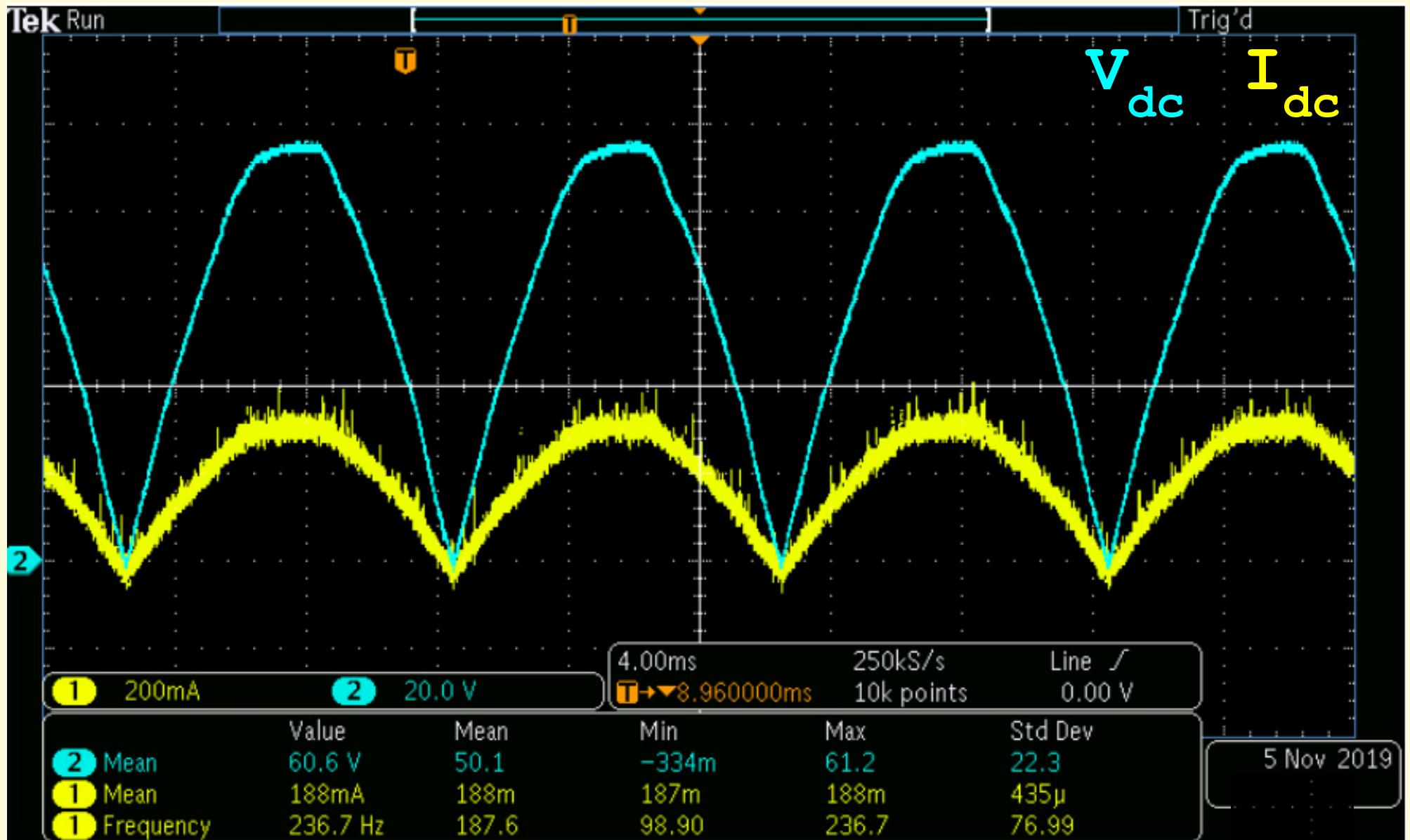

Negative bus not earthed

# Experiment for illustrating isolation


Case-2

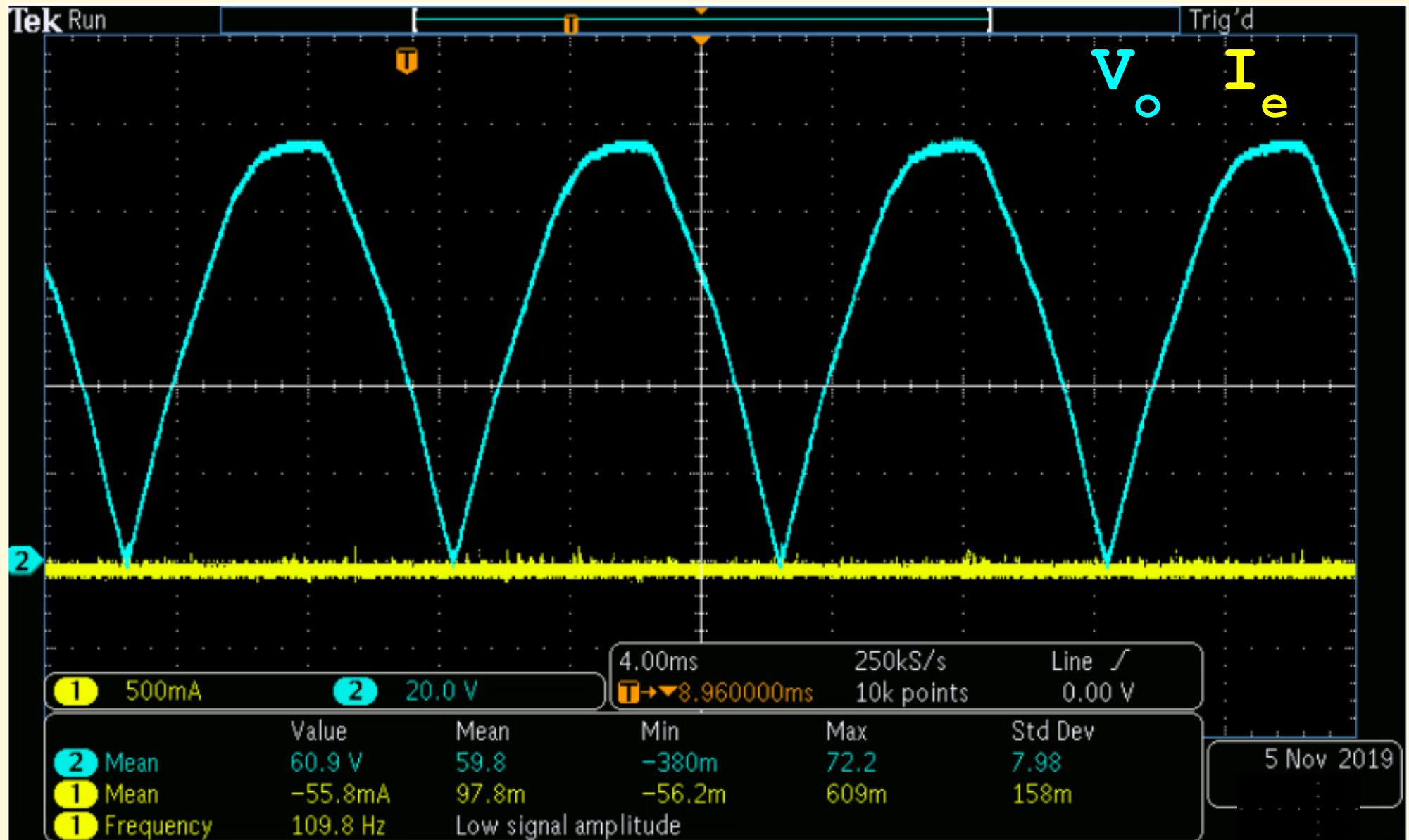


Negative bus earthed through a resistor

# **Three-phase transformer**

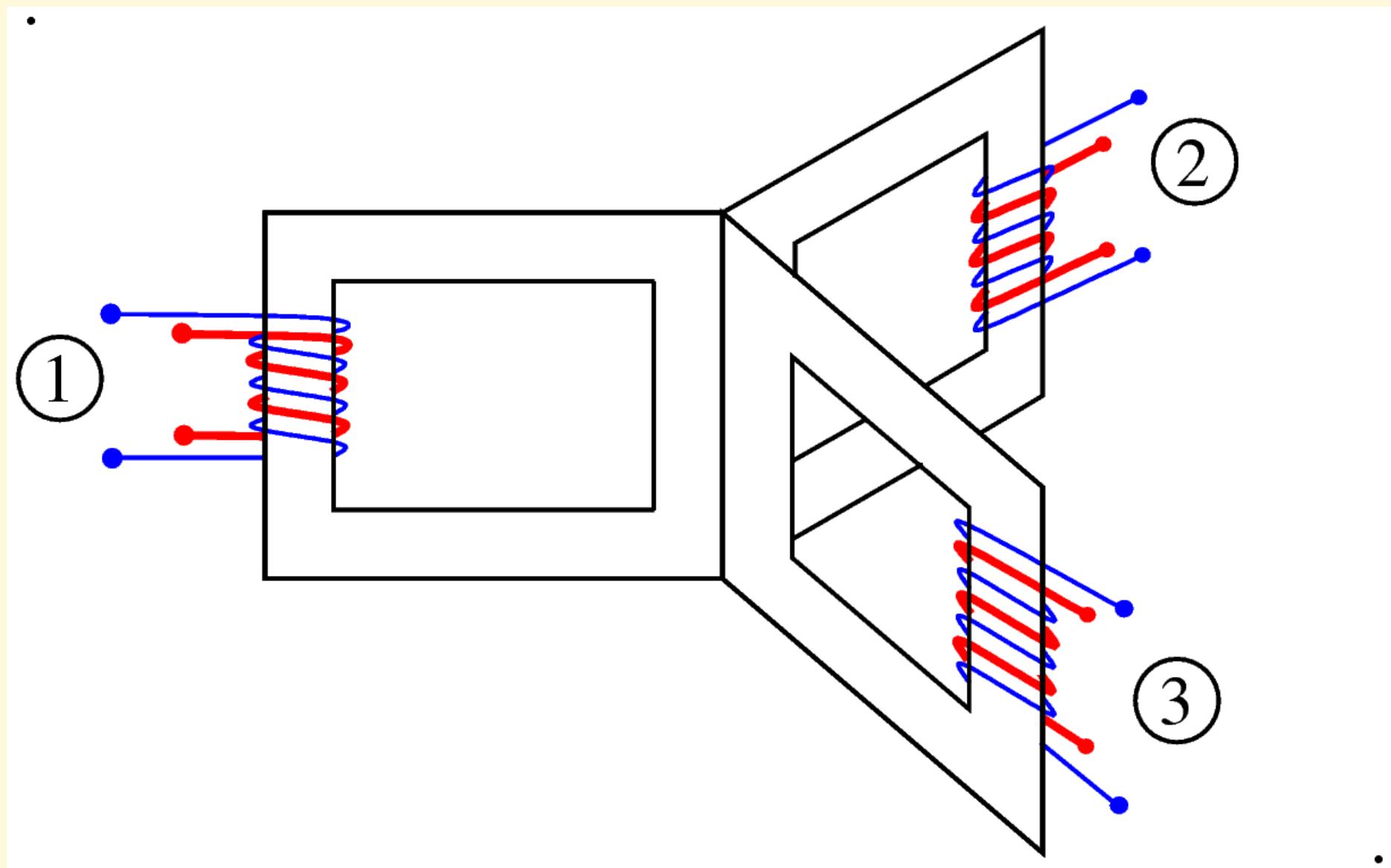
## Three single-phase two winding transformers:


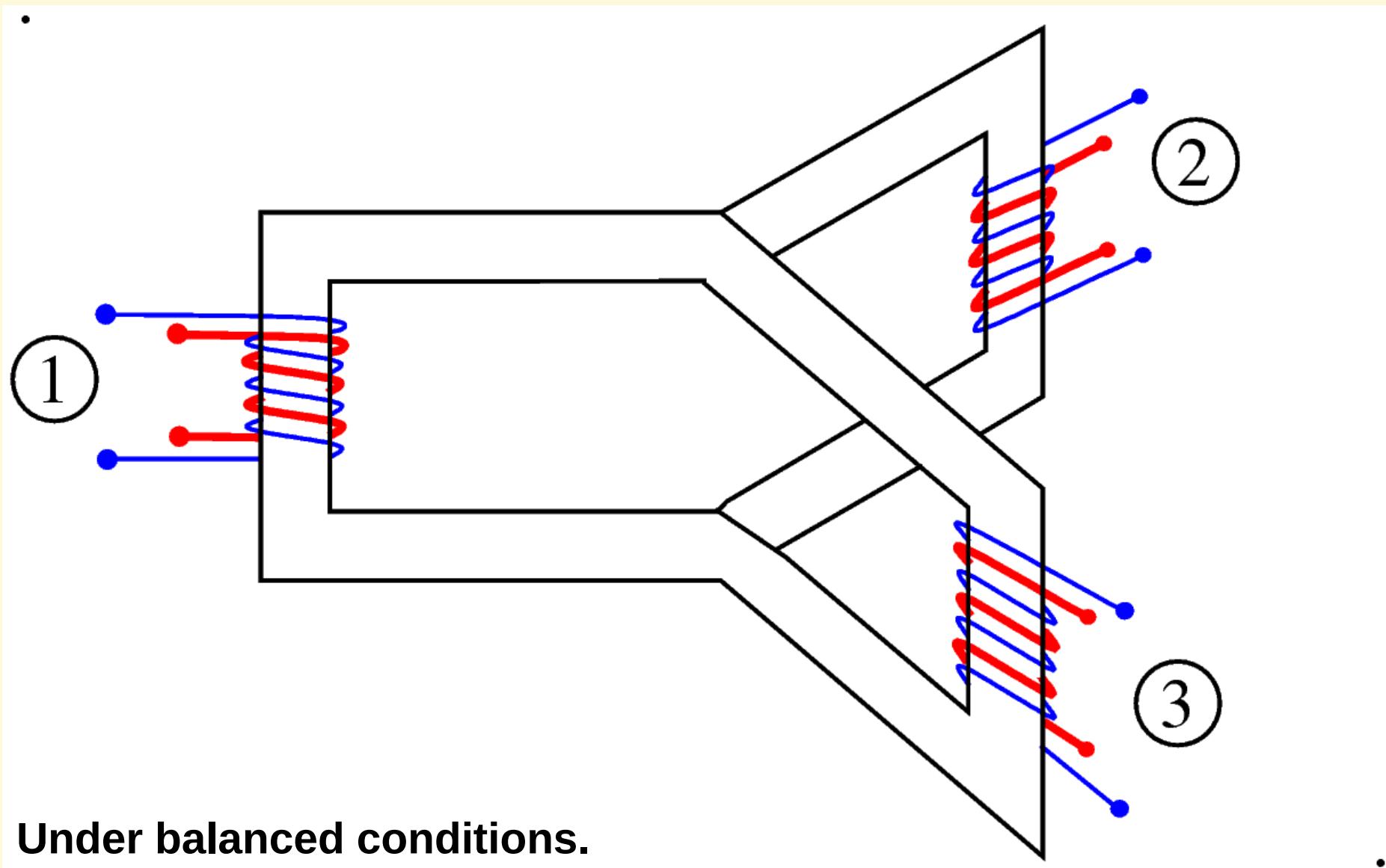
## Three single-phase two winding transformers:






## Three phase two winding transformers:

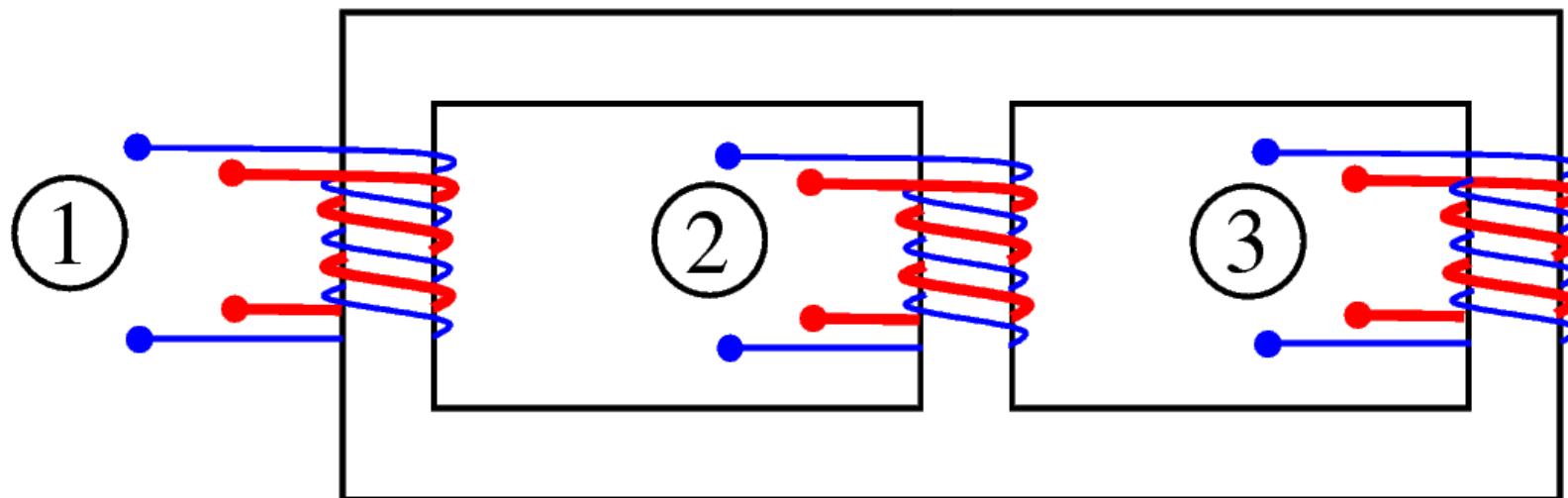

# Three phase (two winding) transformer

Consider the MMF equation:

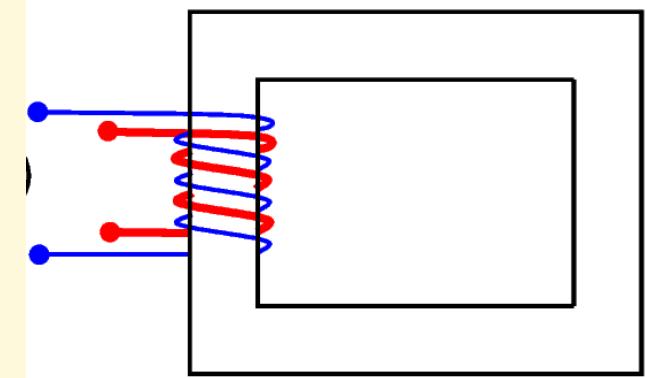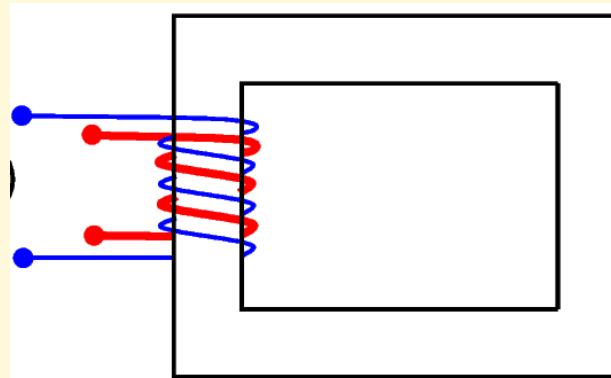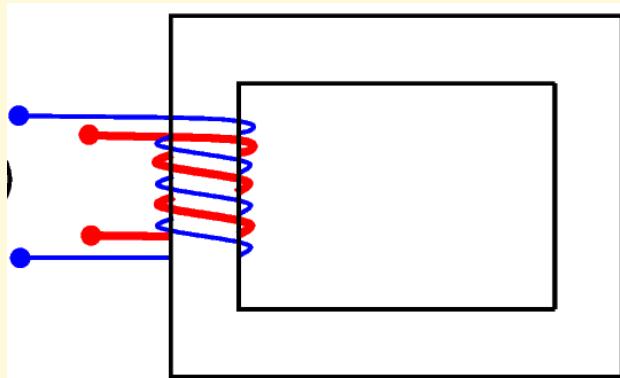

If  $\bar{I}_{oc}$  is **negligible**,


$$N_{lv} \cdot \bar{I}_{lva} + N_{hv} \cdot \bar{I}_{hva} = 0$$

$$N_{lv} \cdot \bar{I}_{lvb} + N_{hv} \cdot \bar{I}_{hvb} = 0$$

$$N_{lv} \cdot \bar{I}_{lvc} + N_{hv} \cdot \bar{I}_{hvc} = 0$$


# Some aspects of three-phase transformer

Consider the following circuit

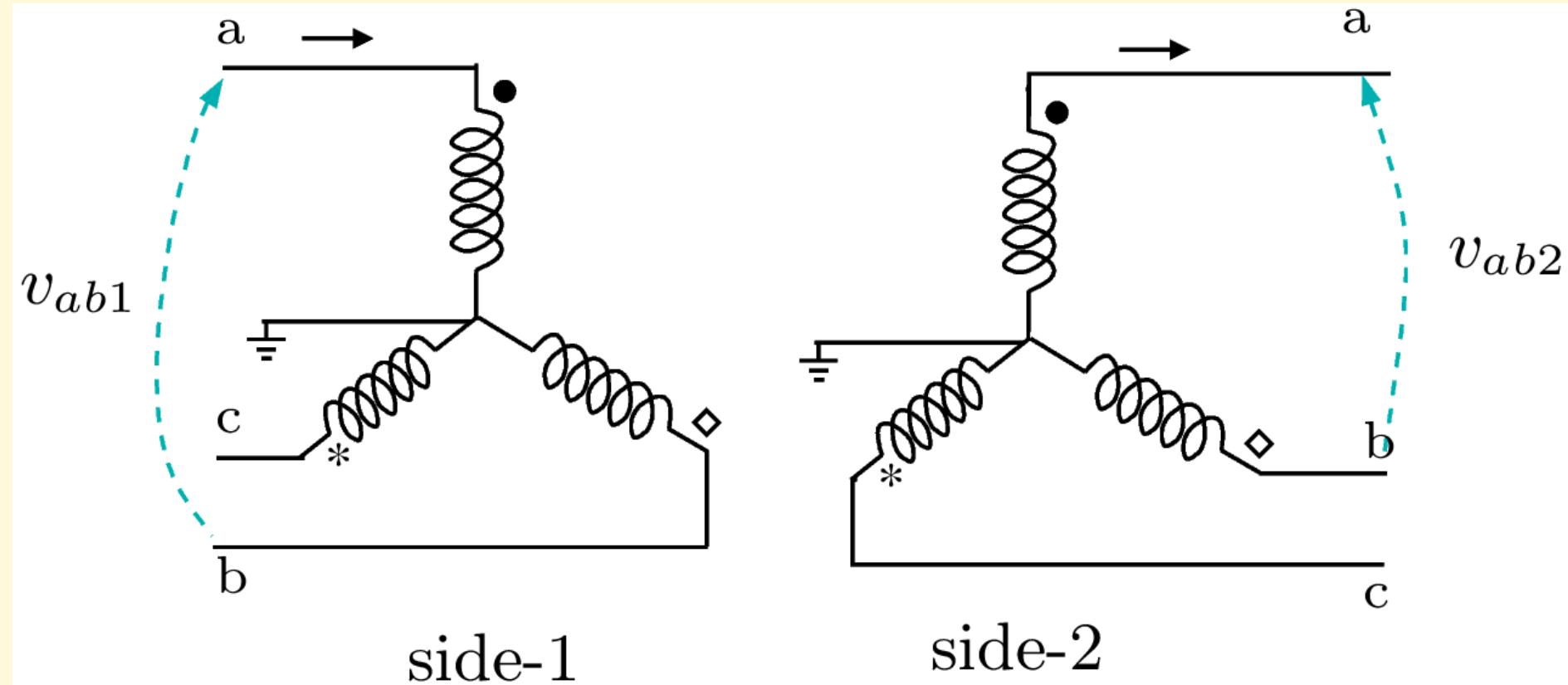

# Some aspects of three-phase transformer

Consider the following circuit

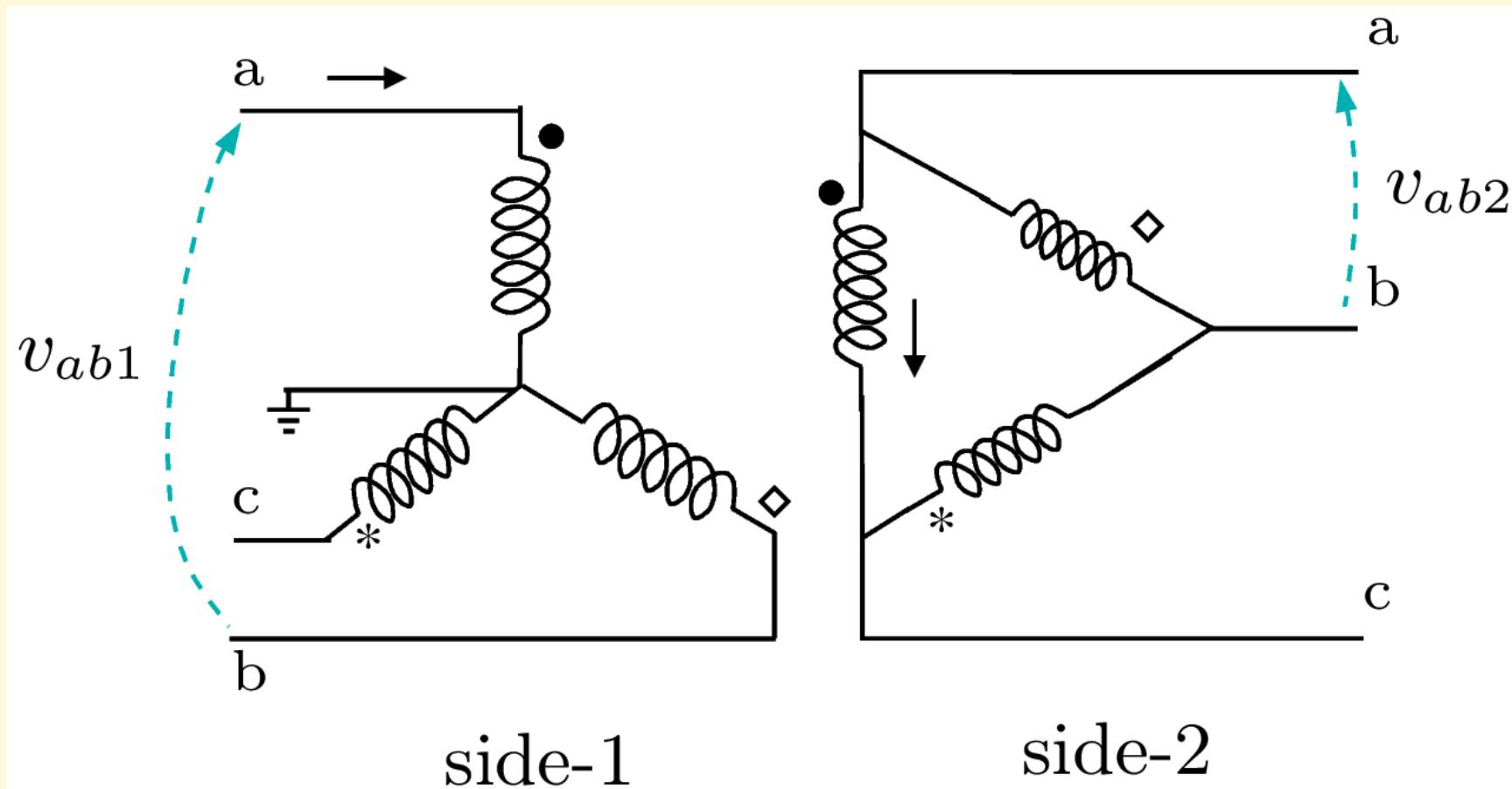

# Some aspects of three-phase transformer

Consider the following circuit

