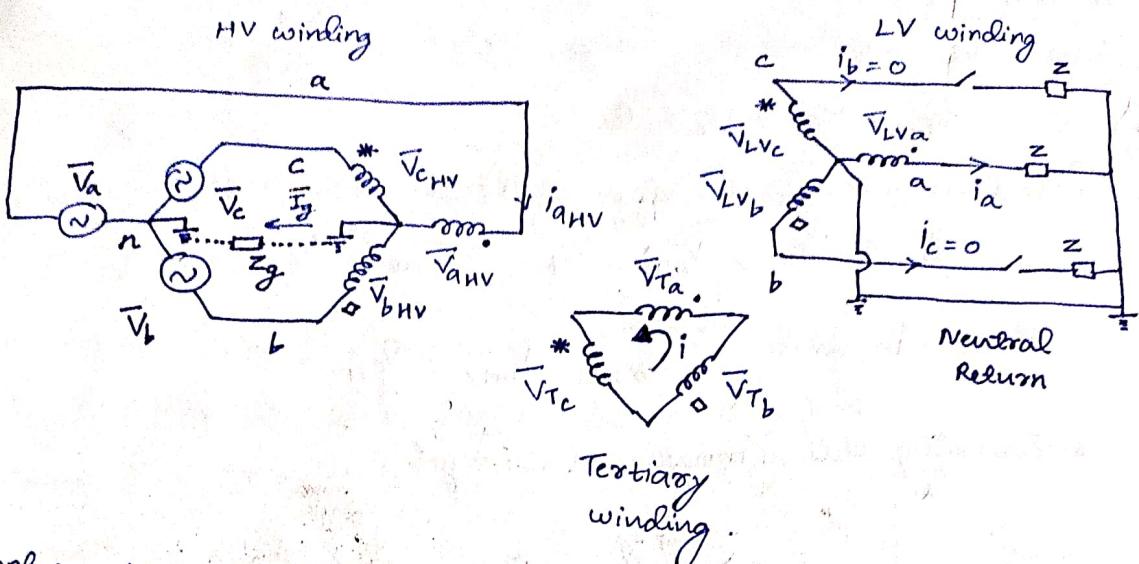


Problem ① :

TUTORIAL 5: A Review of Power Conditioning Circuits



Applying KVL equations to the HV side winding, we get,

$$\bar{V}_a - \bar{V}_{a_{HV}} - \bar{I}_g z_g = 0$$

$$\bar{V}_b - \bar{V}_{b_{HV}} - \bar{I}_g z_g = 0$$

$$\bar{V}_c - \bar{V}_{c_{HV}} - \bar{I}_g z_g = 0$$

Adding the above 3 equations, we get,

$$(\bar{V}_a + \bar{V}_b + \bar{V}_c) - (\bar{V}_{a_{HV}} + \bar{V}_{b_{HV}} + \bar{V}_{c_{HV}}) = 3 \bar{I}_g z_g$$

$$0 - (\bar{V}_{a_{HV}} + \bar{V}_{b_{HV}} + \bar{V}_{c_{HV}}) = 3 \bar{I}_g z_g$$

(since source is balanced,

$$\bar{V}_a + \bar{V}_b + \bar{V}_c = 0$$

$$\bar{V}_{a_{HV}} + \bar{V}_{b_{HV}} + \bar{V}_{c_{HV}} = -3 \bar{I}_g z_g \quad \text{--- ①}$$

Let us assume 'ia' flows through 'a'-winding of LV side.

due to this current, some current 'i' flows through  
Applying KVL to the tertiary winding, we get,

$$\bar{V}_{T_a} + \bar{V}_{T_b} + \bar{V}_{T_c} = 0$$

Since the turns ratio for 3 windings are same, we can say  
 $\bar{V}_{a_{HV}} = \bar{V}_{T_a}$ ,  $\bar{V}_{b_{HV}} = \bar{V}_{T_b}$ ,  $\bar{V}_{c_{HV}} = \bar{V}_{T_c}$

$\therefore$  we can also write,  $\bar{V}_{a_{HV}} + \bar{V}_{b_{HV}} + \bar{V}_{c_{HV}} = 0$

Substituting this in equation ①, we get,

$$0 = -3\bar{I}_g Z_g$$

$$\therefore \bar{I}_g = 0$$

Using per-phase MMF Balance, we can write,

$$\bar{I}_{a_{HV}} + \bar{I} = \bar{I}_a \quad \text{(for phase 'a')}$$

$$\bar{I}_{b_{HV}} + \bar{I} = 0 \Rightarrow \bar{I}_{b_{HV}} = -\bar{I} \quad \text{②}$$

$$\bar{I}_{c_{HV}} + \bar{I} = 0 \Rightarrow \bar{I}_{c_{HV}} = -\bar{I} \quad \text{③}$$

$$\text{we know, } \bar{I}_{a_{HV}} + \bar{I}_{b_{HV}} + \bar{I}_{c_{HV}} = \bar{I}_g = 0$$

Adding equations ②, ③ and ④,

$$\bar{I}_{a_{HV}} + \bar{I}_{b_{HV}} + \bar{I}_{c_{HV}} + 3\bar{I} = \bar{I}_a$$


$$0 + 3\bar{I} = \bar{I}_a$$

$$\therefore \bar{I} = \frac{\bar{I}_a}{3}$$

$$\bar{I}_{b_{HV}} = -\bar{I} = -\frac{\bar{I}_a}{3} \quad ; \quad \bar{I}_{c_{HV}} = -\bar{I} = -\frac{\bar{I}_a}{3} \quad ; \quad \bar{I}_{a_{HV}} = \bar{I}_a - \frac{\bar{I}_a}{3} = \frac{2\bar{I}_a}{3}$$




Problem: 2

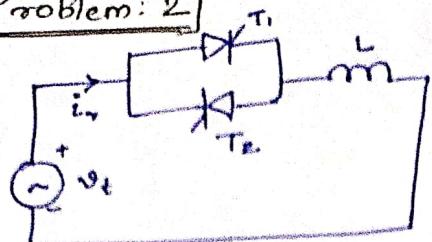

$$L = 500 \text{ mH}$$

Note: here  $90^\circ \leq \alpha \leq 180^\circ$

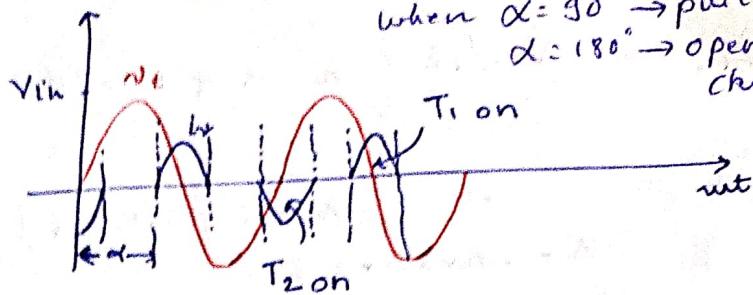when  $\alpha = 90^\circ \rightarrow$  pure L  
 $\alpha = 180^\circ \rightarrow$  open ch.



In order to find expression for fundamental component of current, let us do Fourier analysis. Let  $v_t = V_m \sin \omega t$

Current  $i_r$  for  $1/2$  cycle is given by,

$$i_r = \begin{cases} \frac{V_t}{\omega L} & \text{for } 0 < \omega t < 180 - \alpha \\ 0 & \text{otherwise.} \end{cases}$$

So the fundamental component will be:

$$\begin{aligned} I_{1r} &= \frac{1}{\pi} \left[ \int_0^{180-\alpha} \frac{V_t}{\omega L} \sin \omega t dt + \int_{180}^{180} \frac{V_t}{\omega L} \sin \omega t dt \right] \\ &= \frac{1}{\pi} \left[ \int_0^{180-\alpha} \frac{V_m \sin \omega t \sin \omega t}{\omega L} dt + \int_{180}^{180} \frac{V_m \sin \omega t \sin \omega t}{\omega L} dt \right] \\ &= \frac{V_m}{\pi \omega L} \left[ \int_0^{180-\alpha} \sin^2 \omega t dt + \int_{180}^{180} \sin^2 \omega t dt \right] \\ &= \frac{V_m}{2 \pi \omega L} \left[ \int_0^{180-\alpha} (1 - \cos 2\omega t) dt + \int_{180}^{180} (1 - \cos 2\omega t) dt \right] \\ &= \frac{V_m}{2 \pi \omega L} \left[ \pi - \alpha + \frac{\sin 2\alpha}{2} + \pi - \alpha + \frac{\sin 2\alpha}{2} \right] \\ &\quad @ \frac{V_m}{\pi \omega L} \left[ \pi - \alpha + \frac{\sin 2\alpha}{2} \right] \end{aligned}$$



REV. NOTE 8

@ KUMARAN DEE

It is given that  $I_{1\pi} = 3 \text{ A rms}$

$$I_{1\pi} = \frac{V_m/\sqrt{2}}{\pi wL} \left( \pi - \alpha + \frac{\sin 2\alpha}{2} \right)$$


$$1 = \frac{230}{\pi \times 2\pi \times 50 \times 0.5} \left( \pi - \alpha + \frac{\sin 2\alpha}{2} \right)$$

Solving for  $\alpha$  we get, (using N-R Method)

$\alpha = 2.84^\circ$  or  $162.7^\circ$ . From response:  $\underline{\alpha = 162.7^\circ}$  is the

Solution.

problem ③

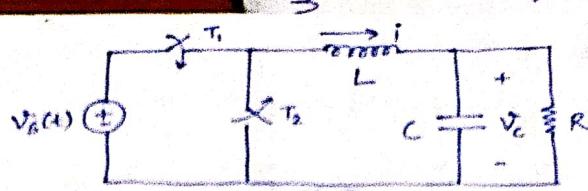

when switch  $T_1$  is ON,

$$L \frac{di}{dt} = V_s(t) - V_C$$

$$i = \frac{CdV_C}{dt} + \frac{V_C}{R}$$

Fig ①

when switch  $T_2$  is ON

$$L \frac{di}{dt} = -V_C$$

$$i = \frac{CdV_C}{dt} + \frac{V_C}{R}$$

since we know that dual of circuit has same equations with voltages replaced by currents and vice-versa , inductors replaced by capacitors , resistances replaced by conductances , loops replaced by nodes and vice-versa , we can write equations for dual of circuit of fig ① as :

when switch  $T_1$  is ON ,

$$C \frac{dV_C}{dt} = i_s(t) - i$$


$$V_C = L \frac{di}{dt} + \frac{i}{G_1}$$

when switch  $T_2$  is ON ,


$$C \frac{dV_C}{dt} = -i$$

$$V_C = L \frac{di}{dt} + \frac{i}{G_1}$$

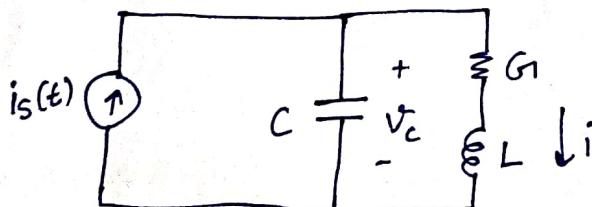
$\therefore$  From above equations (when  $T_1$  is ON) , the equivalent circuit will be :



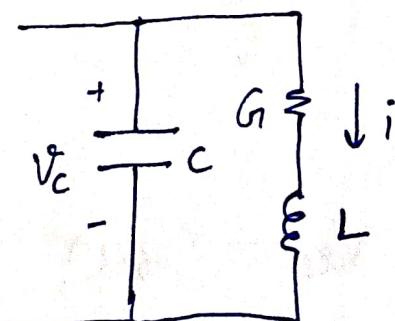From equations (when  $T_2$  is ON and  $T_1$  is OFF) , equivalent circuit will be





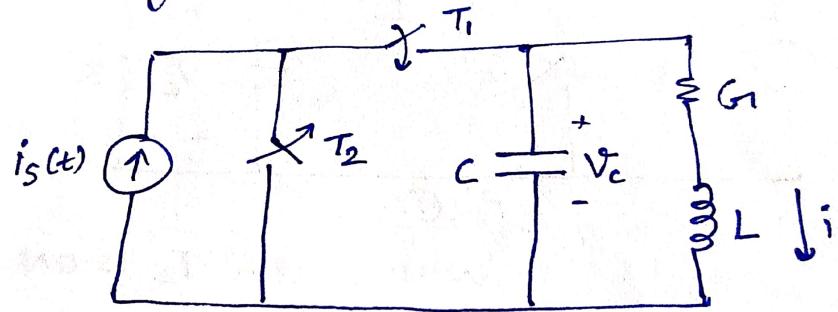Combining above two using  $T_1$  and  $T_2$  switches , circuit will be :



This is the dual of Circuit in fig. ① .

**Problem: 4**

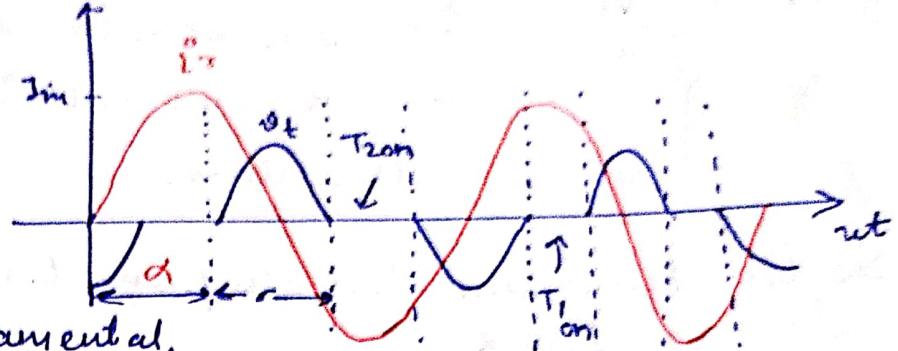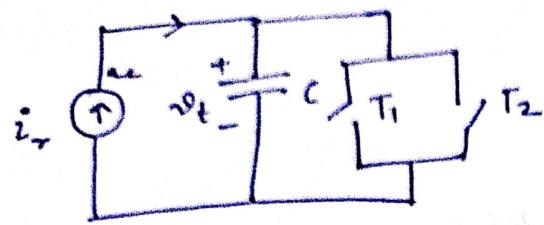

In order to find fundamental,  
we have,

$$v_t = \begin{cases} \frac{ir}{wc} & \text{for } 0 < wt < 180 - \alpha \\ 0 & \text{otherwise,} \end{cases}$$

and  $\alpha < wt < 180^\circ$

Fundamental component will then be,


$$\begin{aligned} V_{it} &= \frac{1}{\pi} \left[ \int_0^{180-\alpha} \frac{ir}{wc} \sin wt dt + \int_{180^\circ}^{180^\circ} \frac{ir}{wc} \sin wt dt \right] \\ &= \frac{Im}{\pi wc} \left[ \int_0^{180-\alpha} \sin^2 wt dt + \int_\alpha^{180^\circ} \sin^2 wt dt \right] \\ &= \frac{Im}{\pi wc} \left[ \pi - \alpha + \frac{\sin 2\alpha}{2} \right] \end{aligned}$$

, put  $\alpha = \pi - \sigma/2 + \theta$   
get expression in terms of  $\sigma$ .

As can be seen from waveform when  $T_1$  or  $T_2$  turns ON, current is not zero, which means switches  $T_1$  and  $T_2$  should have controlled turn off. Thus we should have switches with turn off capability.


3

### Problem 5

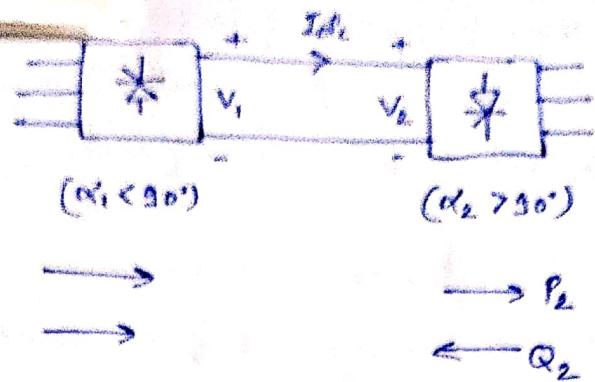


To reverse the direction of power flow, we cannot reverse the direction of current because of presence of thyristors which will not allow reverse current.

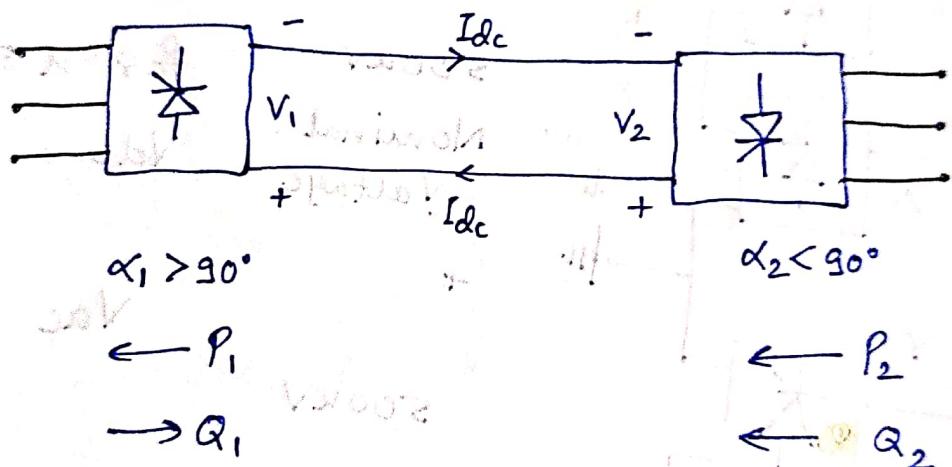∴ We will have to reverse the voltage polarity.



For voltage polarities of  $V_1$  and  $V_2$  as shown in above fig.,  $\alpha_1 > 90^\circ$  and  $\alpha_2 < 90^\circ$ . Reactive power flow directions do not change even if we reverse the active power flow direction.

Problem 5

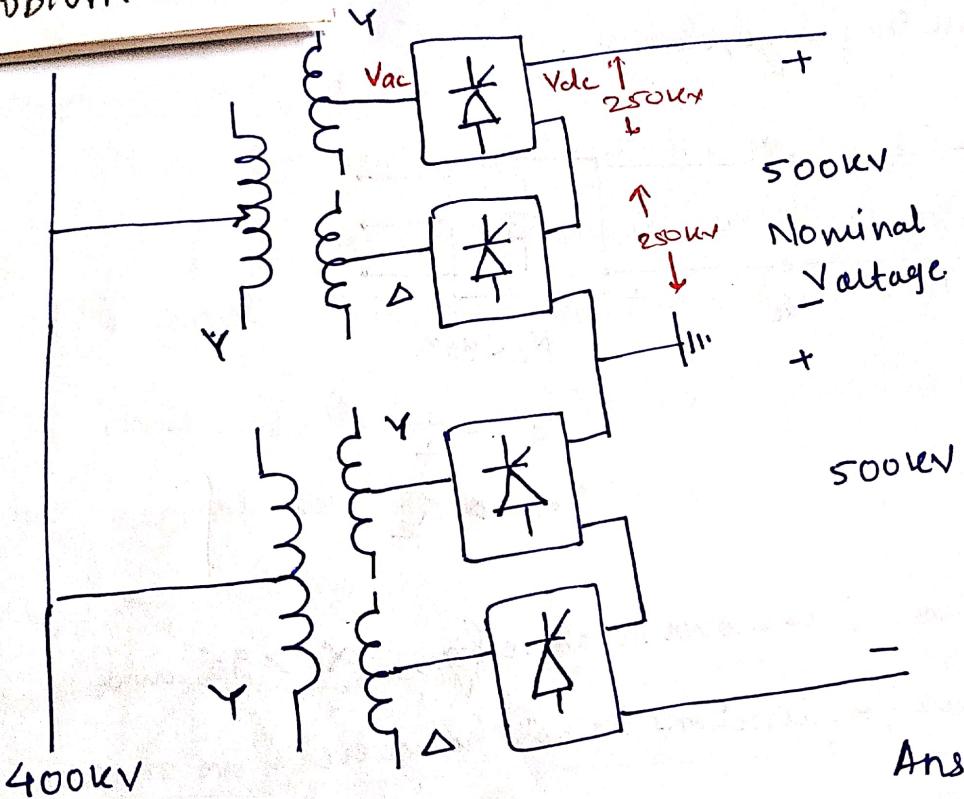

for a thyristor bridge

for  $d = 0^\circ$ ,

$$V_{dc} = \frac{3\sqrt{2} V_{ac}}{\pi}$$

$$V_{ac} = \frac{\pi + 250}{3\sqrt{2}}$$

$$= 185.12 \text{ kV}$$

The nearest AC value  
is 212 kV ( $\alpha \approx 30^\circ$ )

Ans: (a) 400:212

$$\Delta \quad \boxed{4} = \text{the nearest AC value is } 212 \text{ kV } (\alpha \approx 30^\circ)$$

Ans: (a) 400: 212

Problem 7

$$R = 0.75 \Omega, L = 15.2 \text{ mH}, C = 4.2 \mu\text{F}$$


at fundamental frequency (50 Hz)

$$j(X_L - X_C) = j \left( 2\pi \times 50 \times 15.2 \times 10^{-3} - \frac{1}{2\pi \times 50 \times 4.2 \times 10^{-6}} \right)$$

$$= -j753.10 \Omega$$

As  $j(X_L - X_C)$  is negative, so this filter will generate reactive power at the fundamental frequency.

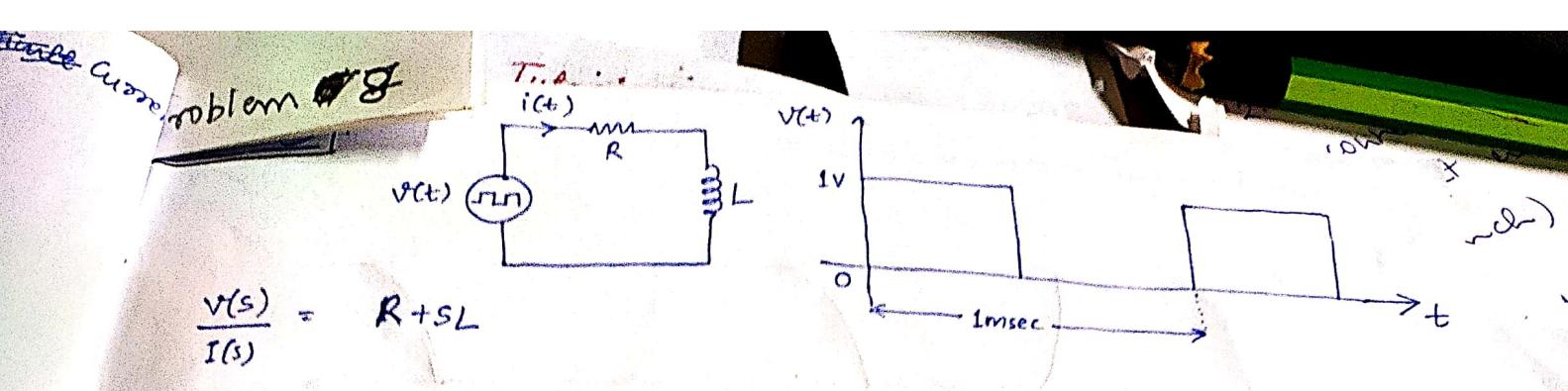Ans: (a) generate reactive power at the fundamental frequency.



$$\frac{V(s)}{I(s)} = R + sL$$

$$\therefore I(s) = \frac{1}{(R + sL)} \cdot V(s) \Rightarrow I(s) = \left(\frac{1}{R}\right) \cdot \frac{1}{(1 + s\tau)} \cdot V(s)$$


a)  $I(s) = \left(\frac{1}{R}\right) \left(\frac{1}{1 + s\tau}\right) \cdot V(s)$

If  $\tau = 1\text{sec}$ , then  $s\tau \gg 1$  (fundamental freq. is 1KHz)

$$\therefore I(s) \approx \left(\frac{1}{R}\right) \cdot \frac{1}{s\tau} V(s) = \frac{1}{s\tau} V(s) = \frac{V(s)}{s}$$

$$\therefore i(t) \approx \int V(t) dt$$

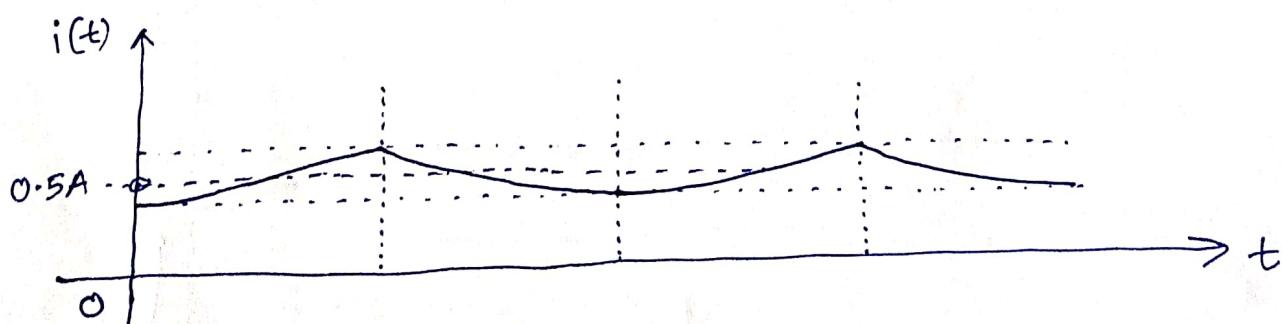$\therefore$  Current waveform will approximately be as shown below :



b)  $I(s) = \left(\frac{1}{R}\right) \left(\frac{1}{1 + s\tau}\right) \cdot V(s)$


If  $\tau = 1\mu\text{sec}$ , then  $s\tau \ll 1$ ,

$$I(s) \approx \left(\frac{1}{R}\right) \cdot V(s) \approx V(s)$$



REDMINE  
@KAUSTAVDEY

i: Current waveform in this case will be :

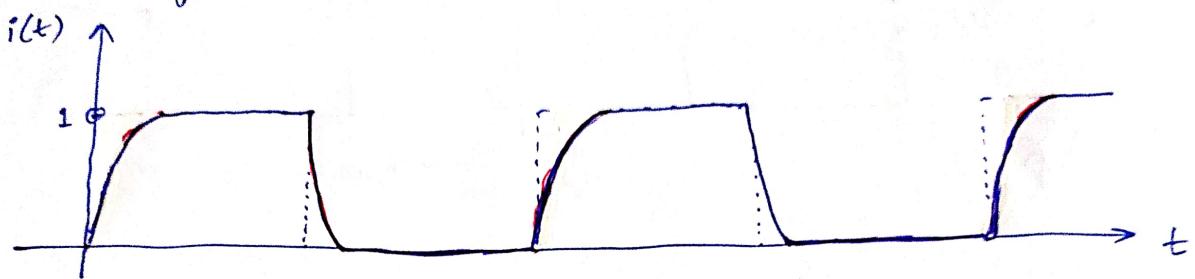


Problem 9

RMS value of fundamental component of voltage ,

$$V_{1\text{rms}} = \frac{4 \times 240}{\pi \times \sqrt{2}} = 216.11 \text{ volt} .$$


$$Z(\text{at fundamental}) = R + j\omega L = 10 + j(2\pi \times 50 \times 0.06) = 10 + j18.85 \Omega$$

$$\therefore I_{1\text{rms}} = \frac{V_{1\text{rms}}}{|Z|} = \frac{216.11}{\sqrt{(10)^2 + (18.85)^2}} = 10.13 \text{ A}$$

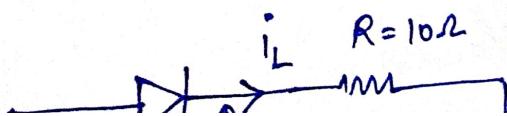

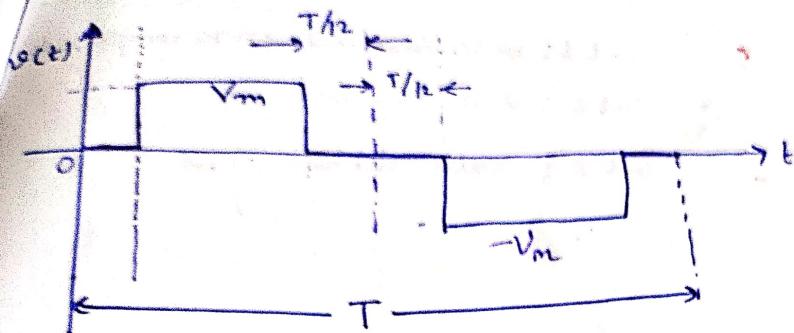Problem 16

Any periodic signal can be represented as sum of sinusoidal signals.



The expression for voltage  $v(t)$  after doing Fourier analysis is given by,

$$v(n) = \frac{4V_m}{n\pi\sqrt{2}} \cos(n\pi/6)$$


where  $v(n)$  is  $n$ th component of voltage.

for  $n=3$ ,

$$v(3) = 0$$

~~REMEMBER~~ ~~the magnitude of the 3rd harmonic component will be zero.~~

Problem: 11

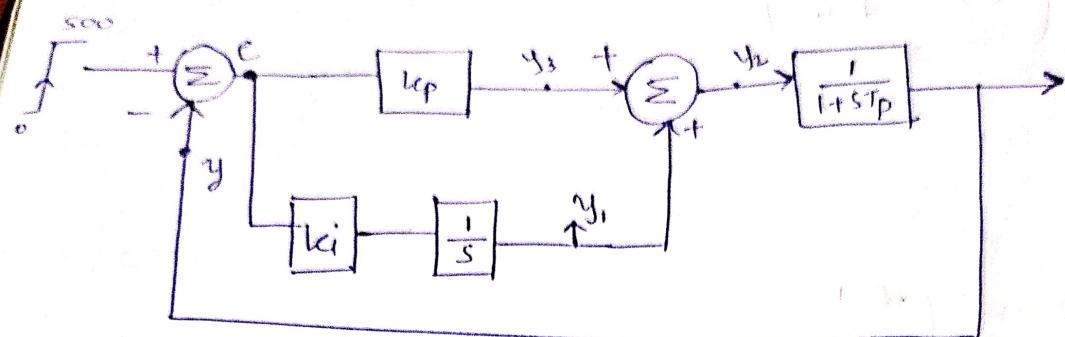

We know that steady state error = 0 for PI controller, thus,  
 $e = 0$ , which means  $y_2 = 500$  at steady state.

At steady state gain of  $\frac{1}{1+sT_p} = 1$  thus,  $y_2 = 500$

$$y_2 = y_3 + y_1$$

$$y_3 = e \times k_p = 0, \text{ thus } y_2 = y_1 = 500$$

Thus at steady state  $y_1 = 500$ .

Problem : 12

$$G(s) = \frac{5(1+0.136s)}{(1+0.01s)(1+0.1s)}$$

The poles are  $s = -10, -100$

clearly the systems are well separated with one fast mode (-100) and one slow mode (-10). So initial response will be only due to  $s=100$  and steady state will be due to both poles.

Using partial fractions,

$$G(s) = \frac{4}{1+0.01s} - \frac{2}{1+0.1s}$$


So response will go towards 4 in  $5\tau_1$  (0.05s). Then finally it will reach steady state (5) in  $5\tau_2$  (0.5s).

(b) option 2 is correct.




REDMI NOTE 8  
@KAUSTAVDEY

(a) Given

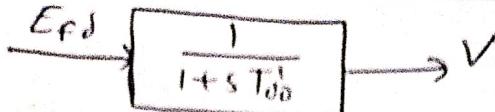


$$\text{and } T_{do} = 5 \text{ s.}$$

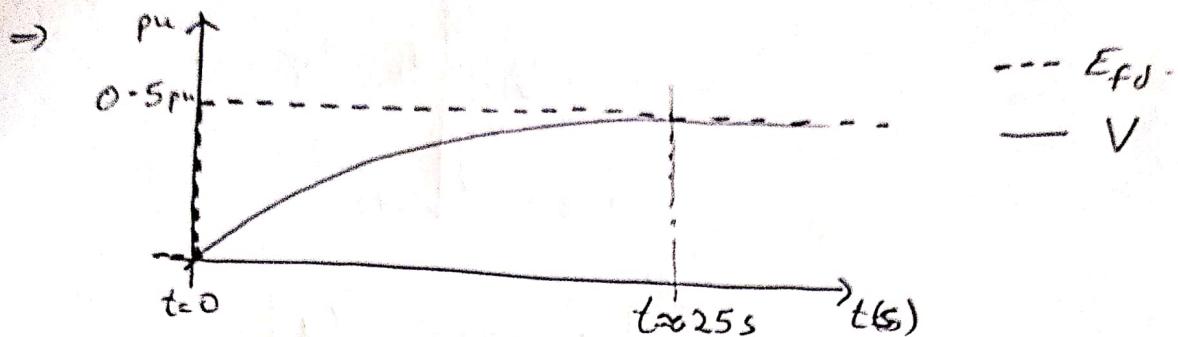

⇒ [Note: here pu refers to per unit.  $0.5 \text{ pu}$  refers to 50% of the rated voltage or quantity] //

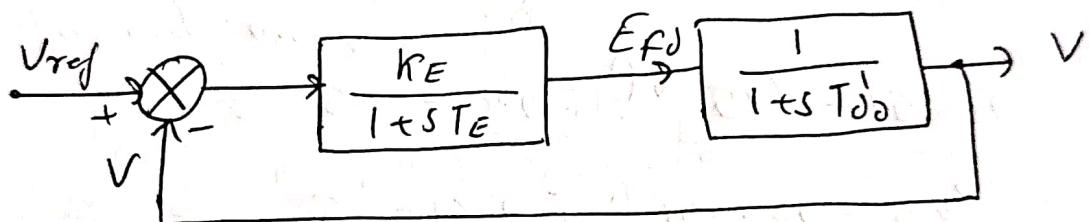(b) If the  $E_{fd}$  is controlled as shown



$$\text{Here } C(s) = \left( \frac{K_E}{1 + sT_E} \right) \cdot \left( \frac{1}{1 + sT_{do}} \right)$$

$$\text{and } H(s) = 1$$

$$\text{Here } T_E = 0.045$$

∴ Closed loop poles of above system

$$1 + C(s) H(s) = 0$$

$$\therefore s^2 + 25.2s + 5(1 + K_E) = 0 \quad \text{--- (1)}$$

→ To determine  $K_E$  such that the poles are complex conjugates and with damping ratio 10%.

$$\therefore s = -12.6 \pm j\sqrt{5k_E - 153.76}$$

Comparing with

$$\boxed{\sigma = -12.6} \quad s = \sigma + j\omega \quad \text{and} \quad \boxed{\omega = \sqrt{5k_E - 153.76}}$$

$\therefore$  Substituting these values in eq<sup>n</sup> ② we get,

$$\boxed{k_E = 3174.2}$$

Term: 14

Steady state gain = 1. High frequency gain =  $\frac{T_1}{T_2} < 1$ . So after step is applied, the initial response will be  $< 1$  and then it will reach 1 with time constant  $T_2$ . So (c) option is correct.

